



**DO NOT SHARE
SLIDES AND CLASS MATERIALS
ON ONLINE SITES**

Course Hero


Advanced Logic Design

FPGA

Mingoo Seok
Columbia University


(1) BV: Secs. B.6, B.10; (2) J. F. Wakerly “Digital Design: Principles and Practices,” 4th Edition, Prentice Hall (2006), pp.850-862

Programmable Logic Array


 


- A early version of FPGA, which allows users to program a rather complicated logic function in a single chip


General Structure of a PLA

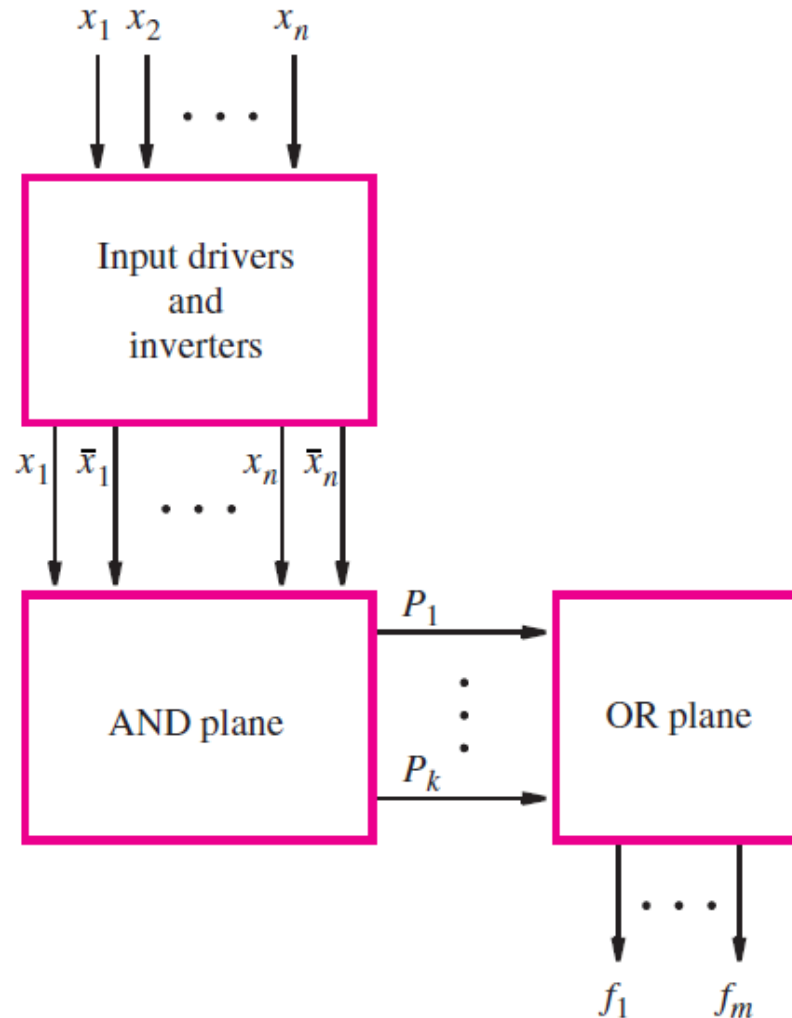

PLA: Detail

 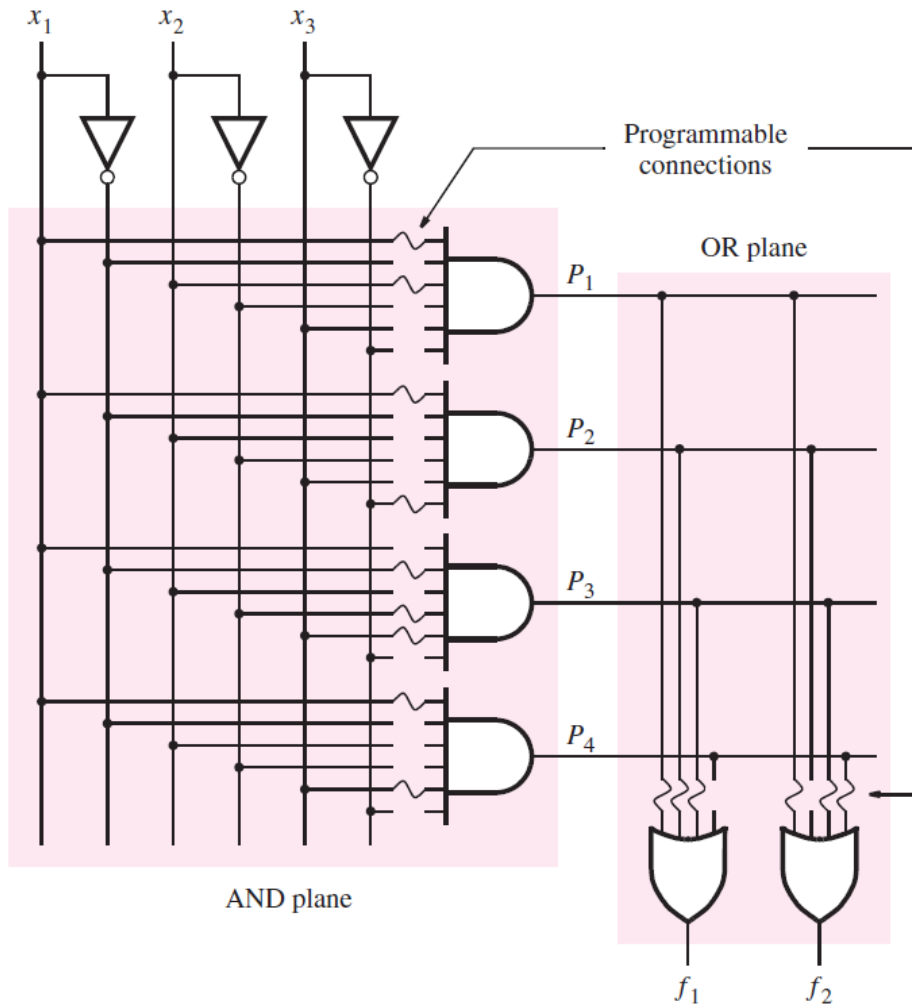


NOR-NOR PLA

 


- NOR is preferred for large fan-in gates
- Resistor-load is preferred over CMOS


F(ield)PLA

 

(a) Programmable NOR-plane

 


(b) A programmable switch

 


(c) EEPROM transistor


PAL: Programmable Array Logic

 


- The AND plane is programmable but the OR plane is fixed.
- To relieve the fabrication complexity of programmable switches

Complex PLD

 


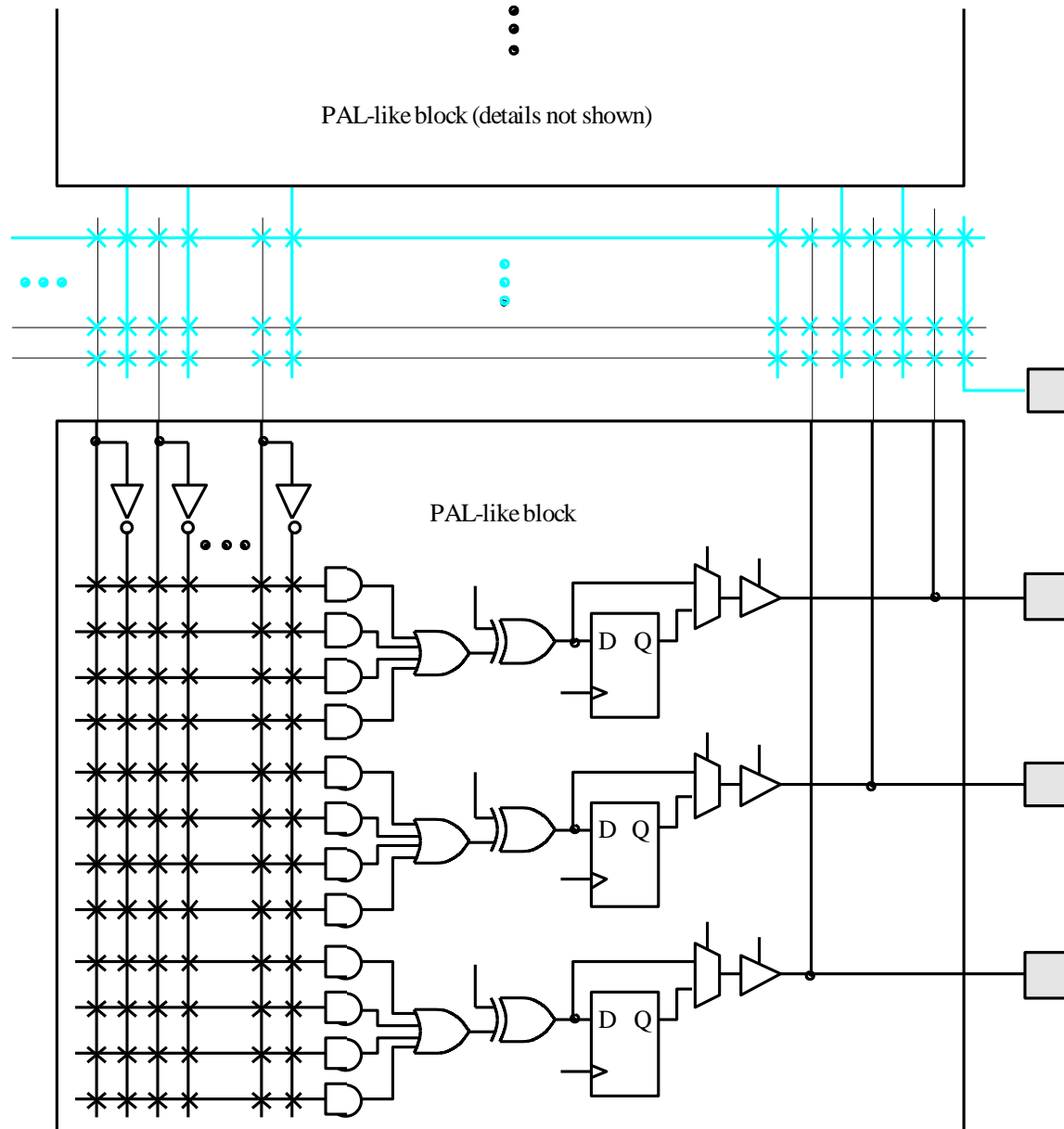

Field Programmable Gate Array

 


LUT for Logic Function

 


- 3 inputs: 8-W latches
- 4 inputs: 16-W latches
- 5 inputs: 32-W latches
- Granularity vs overhead \rightarrow 4 to 6 inputs are commonly found


Another LUT Implementation

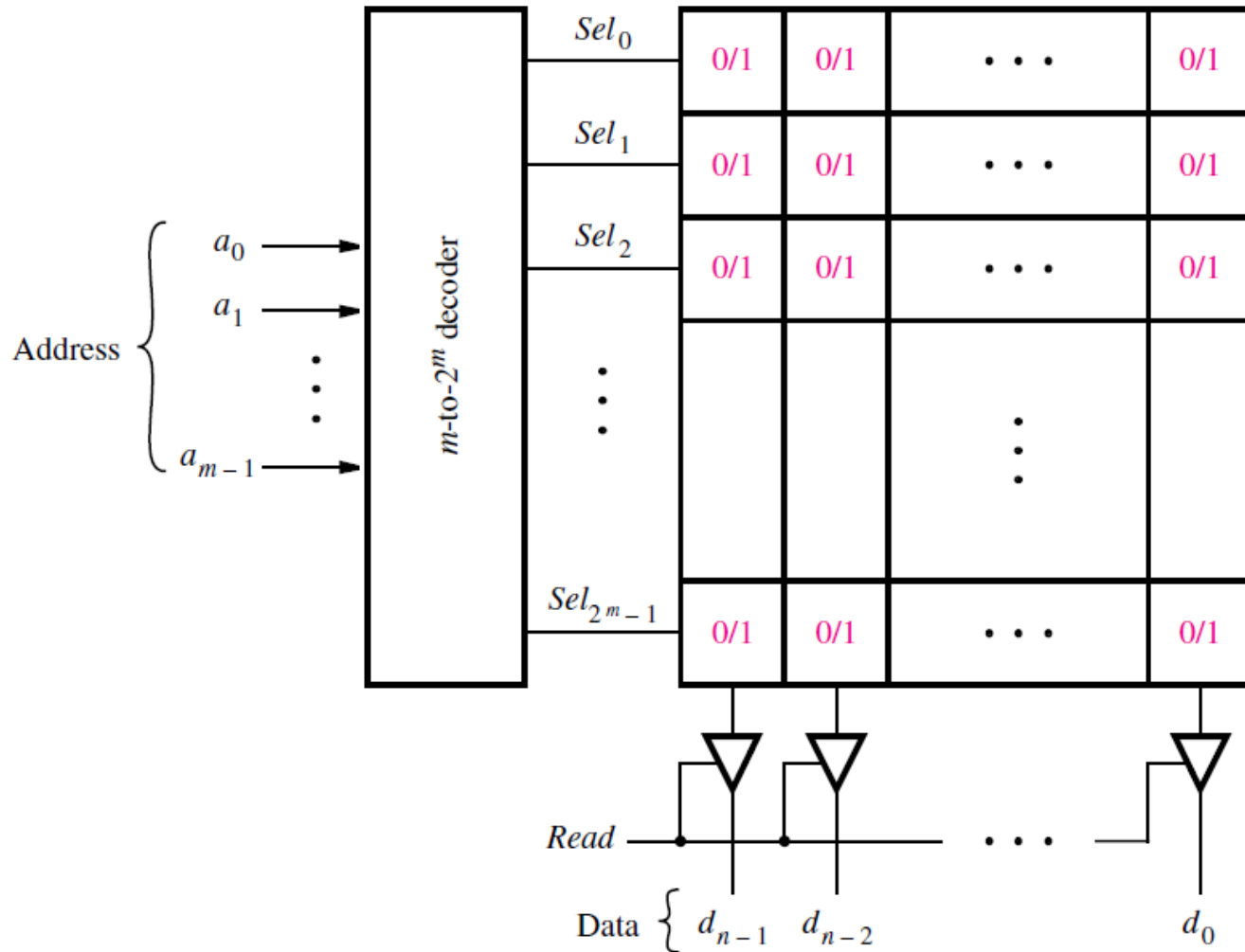


Pipelining/Sequencing

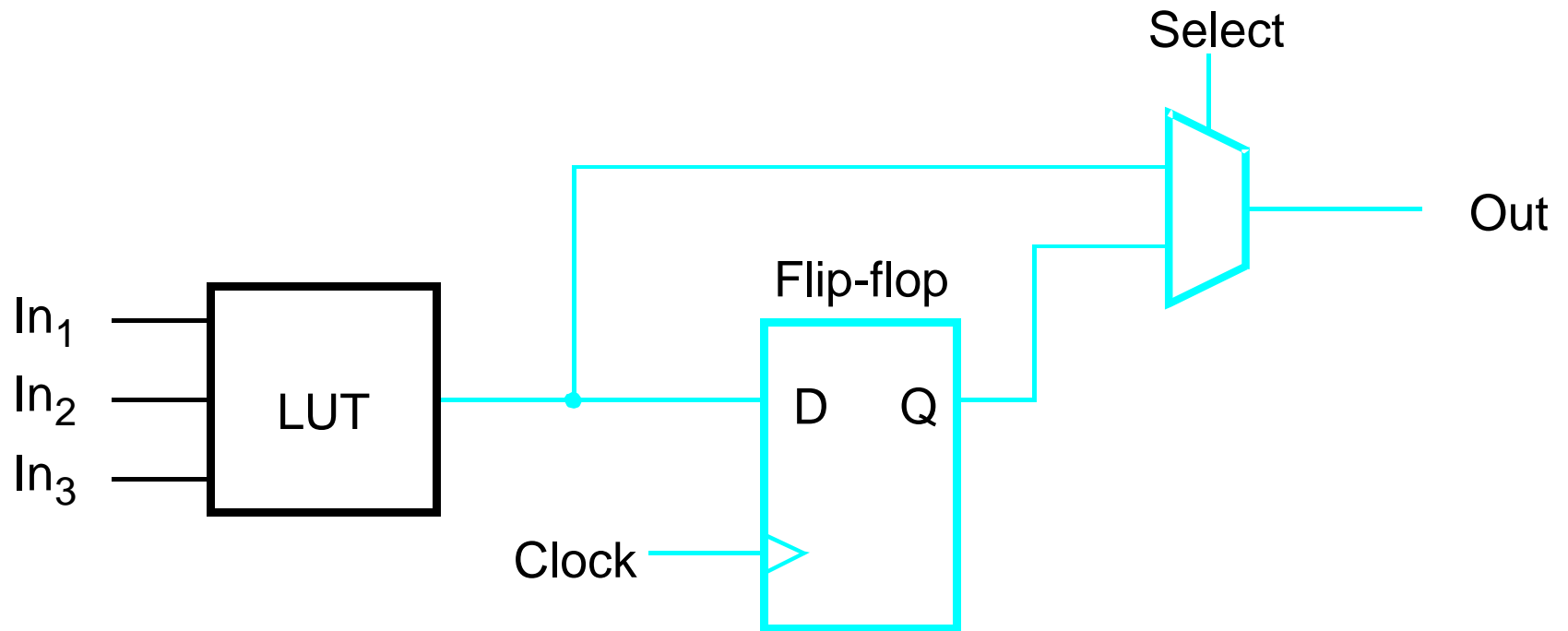

Configurable Logic Block (CLB)

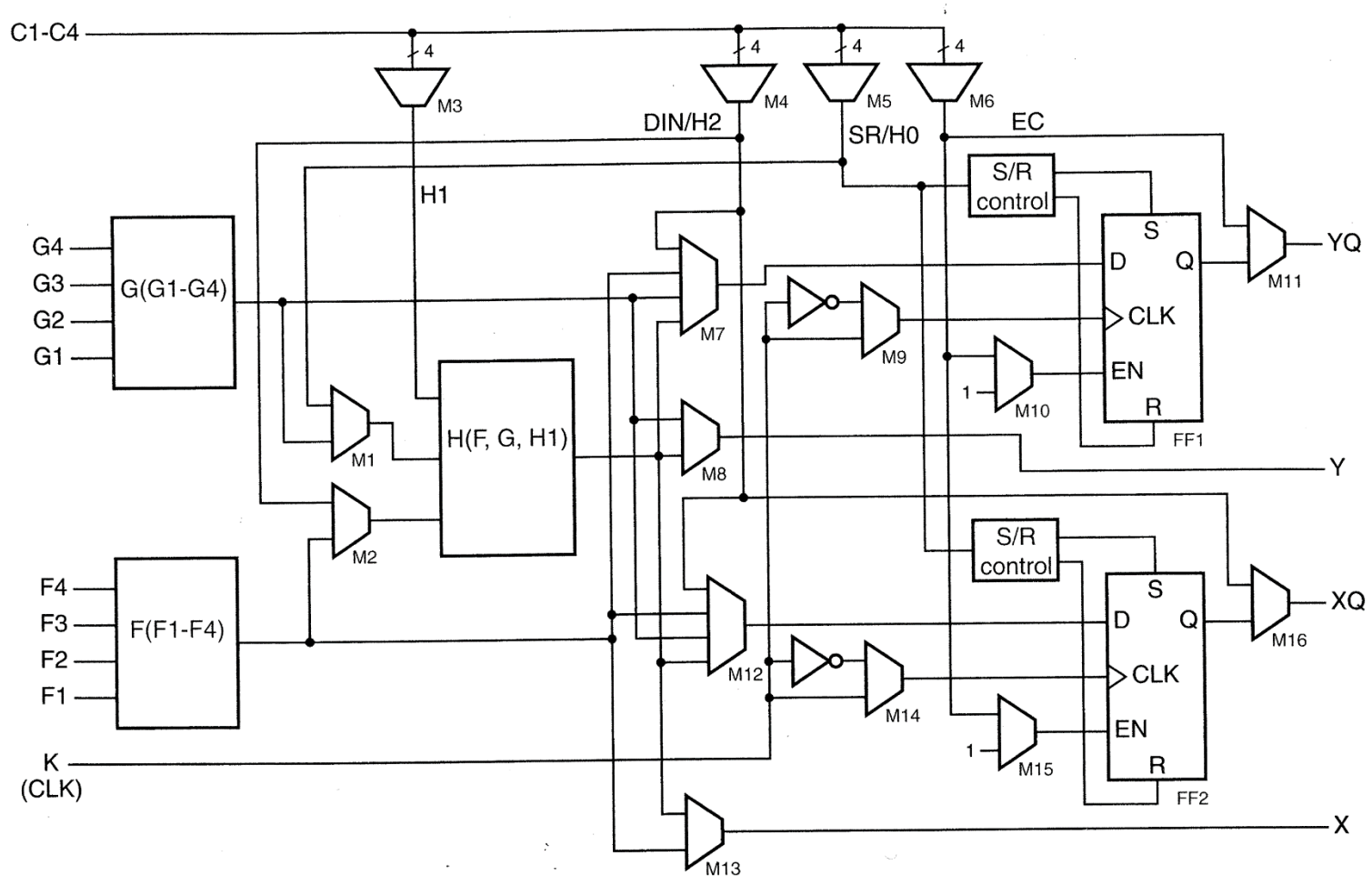


Configurable Logic Block (CLB)

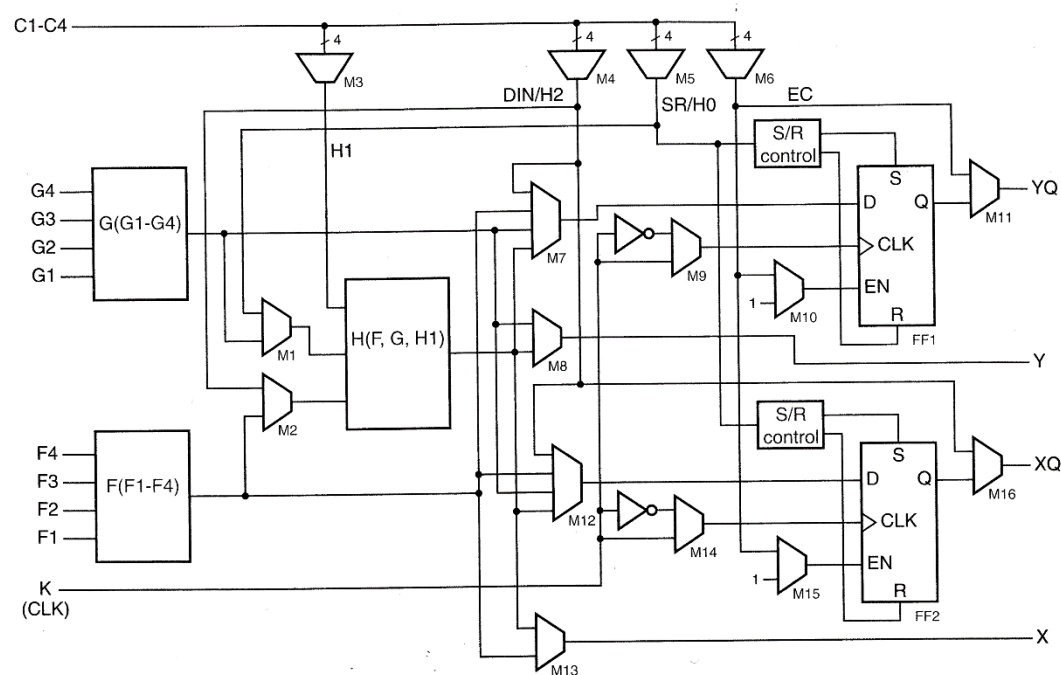


- 12 inputs, 4 outputs, 1 clock
- Three LUTs (G, F, H); 4-input and 3-input
- M9, M14 for rising, falling edge selection
- S/R: set and reset control
- Clocked and non-clocked output support
- LUTs can be programmed as a data storage during the start-up

IO Block

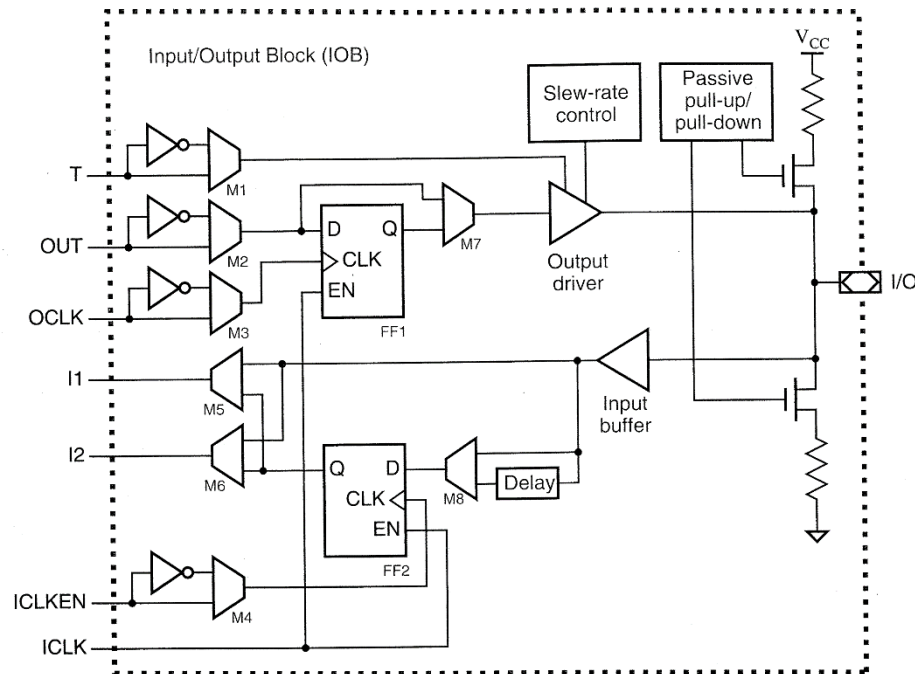


- M5, M7: clocked input and output selection
- Delay: slow down the input data relative to ICLK (FPGA internal clock) to avoid hold time violation
- M1-M4: polarity inversion
- Analog control: slew rate and passive pull-up and –down selection

Interconnect

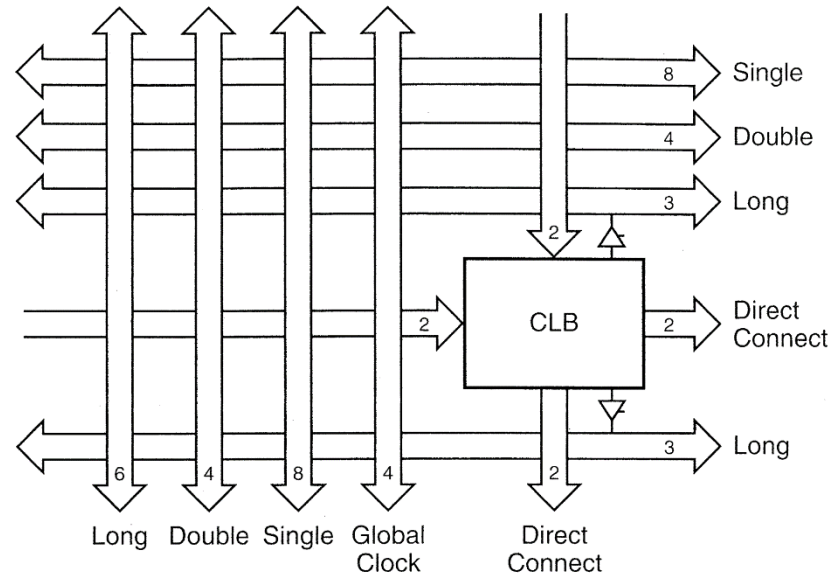


- Direct: direct connection to nearby CLBs; unidirectional
- Double and single: respectively have hops (programmable switches) in every two and every CLBs
- Long: data travels all the way across a row or a column without hops, and driven by tri-state drivers near CLBs (something like a bus)


Interconnect

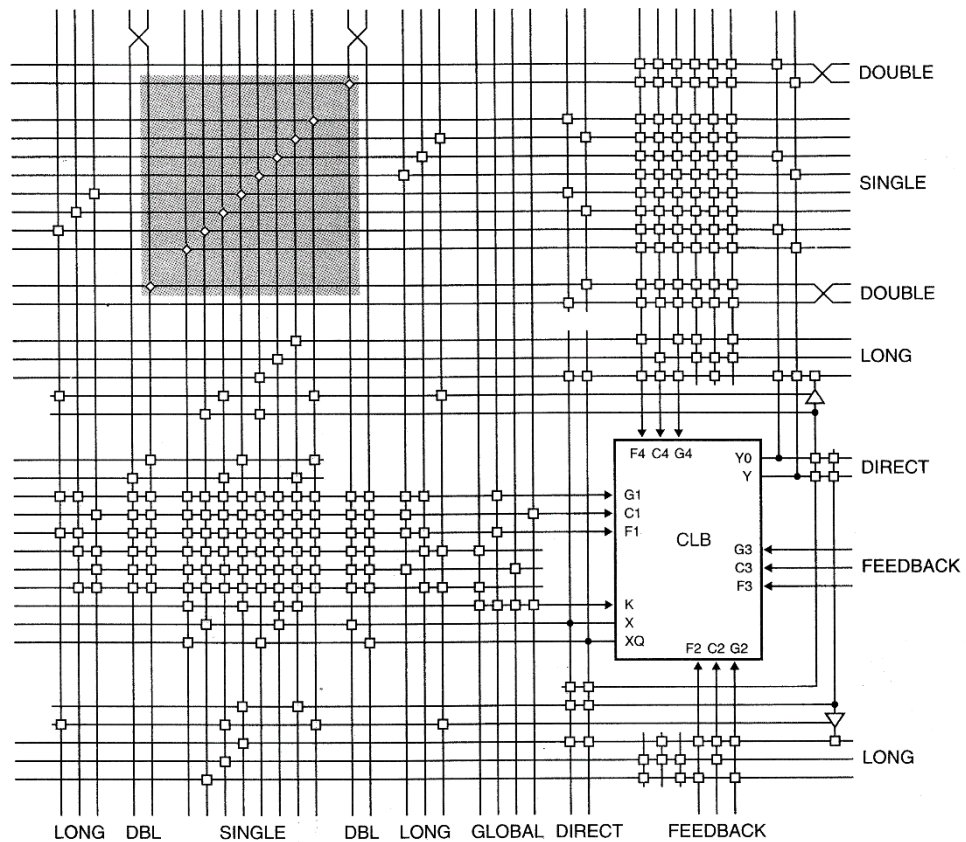

Connecting Interconnects

 


PSM: Programmable Switch Matrix

 

- Connecting the four wires in various ways
- Six exemplary connections

FPGA Programming Example

 

- $f_1 = ?$
- $f_2 = ?$
- $f = ?$