

# Advanced Logic Design

## Lecture 2: Combinational Logic Circuits Refresher

Mingoo Seok  
Columbia University

BV: Sec. 2.1-2.8, 2.11-2.22


# Logic Circuits

- Logic circuits: in which the signals are constrained to have only some number of discrete values
- Binary logic: only two values, 0 and 1
  - Other logic circuits exist: e.g., ternary (-1,0,+1)
  - But binary logic has an advantage in robust and scalable VLSI hardware implementation


# Binary Switch




(a) Two states of a switch

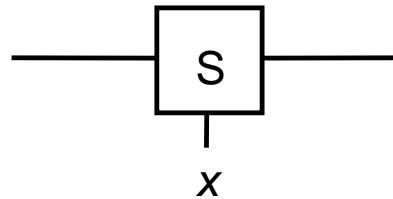


(b) Symbol for a switch

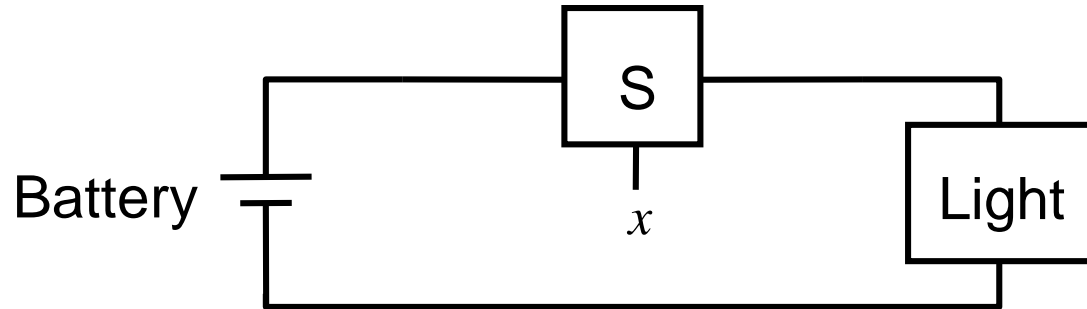

(a) Simple connection to a battery

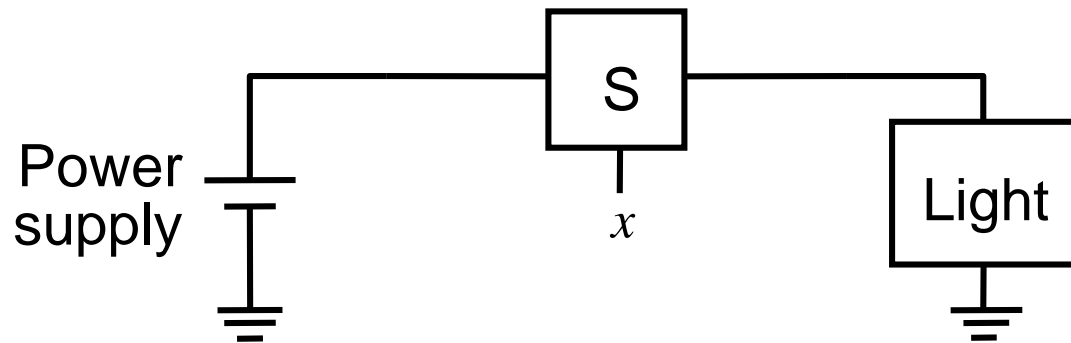

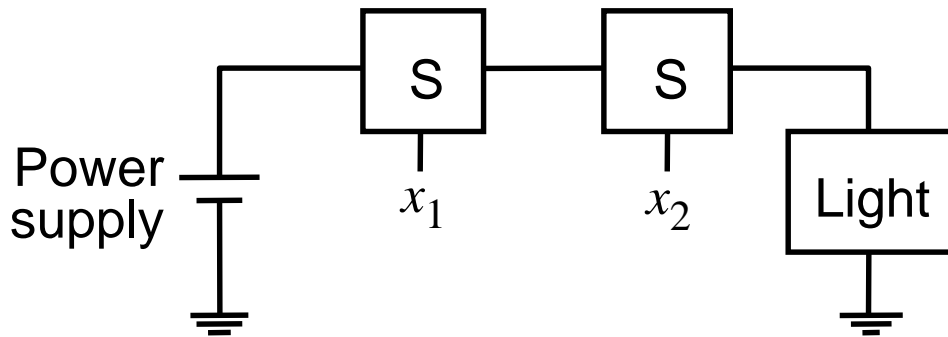
(b) Using a ground connection as the return path



$$L(x_1, x_2) = x_1 \cdot x_2$$

where  $L = 1$  if  $x_1 = 1$  and  $x_2 = 1$ ,  
 $L = 0$  otherwise.

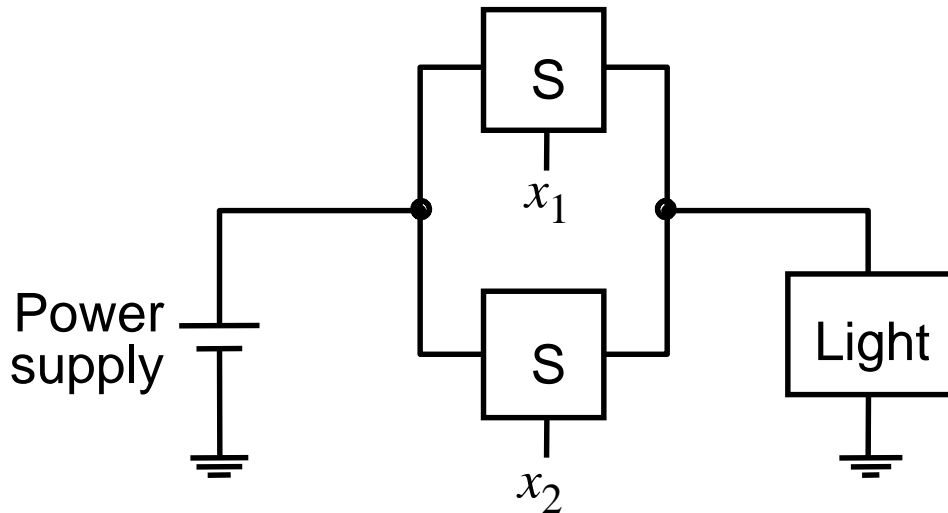
(a) The logical AND function (series connection)



$$L(x_1, x_2) = x_1 + x_2$$


where  $L = 1$  if  $x_1 = 1$  or  $x_2 = 1$  or if  $x_1 = x_2 = 1$ ,  
 $L = 0$  if  $x_1 = x_2 = 0$ .

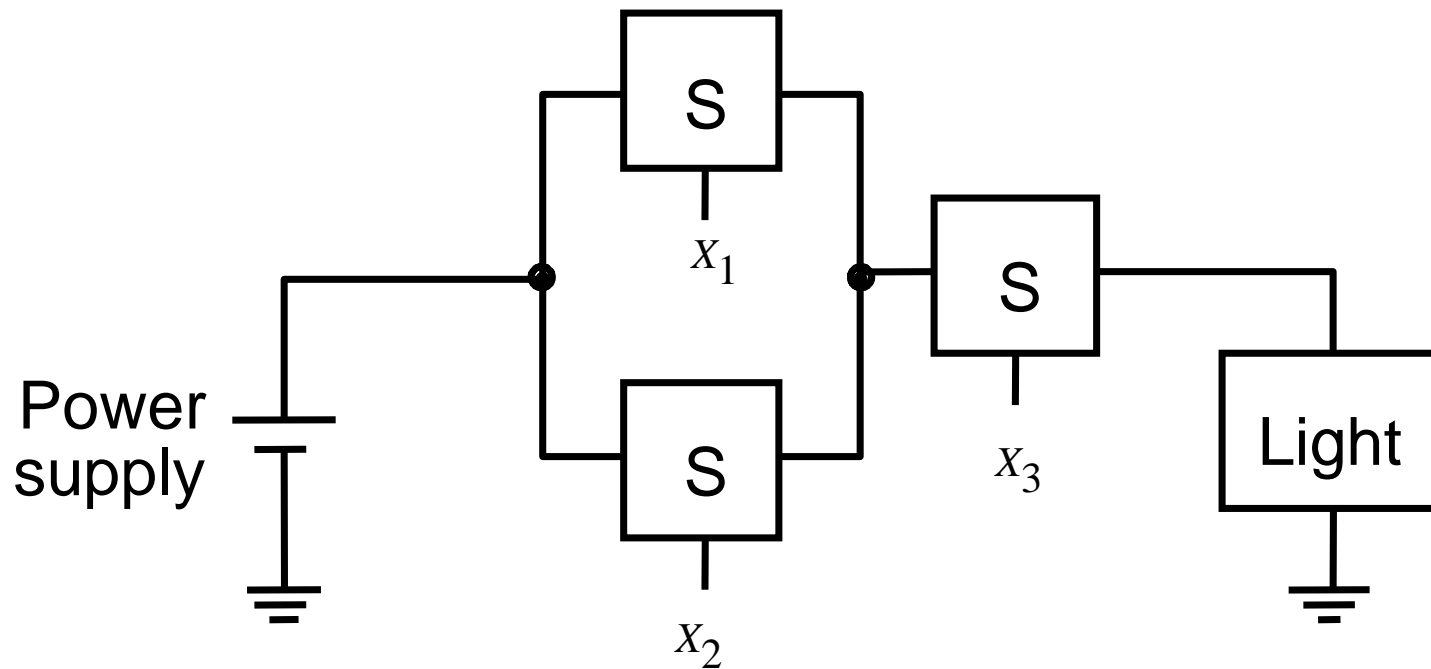(b) The logical OR function (parallel connection)



$$L(x_1, x_2, x_3) = (x_1 + x_2) \cdot x_3$$

# Inversion

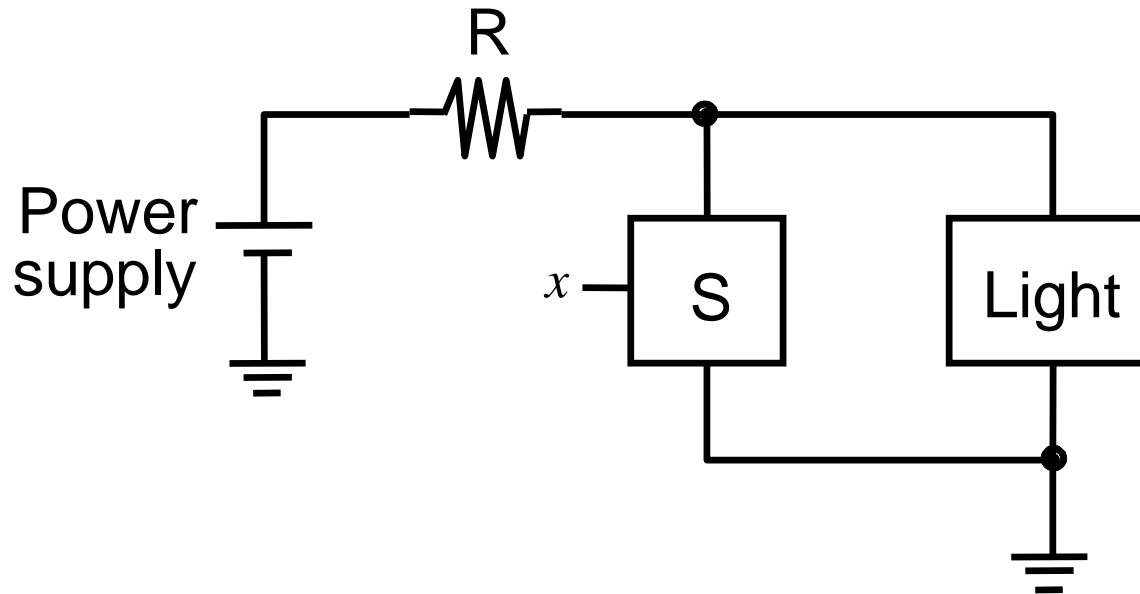

$L(x) = \bar{x}$   
where  $L = 1$  if  $x = 0$ ,  
 $L = 0$  if  $x = 1$

$$\bar{x} = x' = !x = \sim x = \text{NOT } x$$

- The switch will short-circuit the light and prevent the current from flowing through it
- Inverse = complement = NOT

# Truth Table


$x_1$	$x_2$	$x_1 \cdot x_2$	$x_1 + x_2$
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	1

AND      OR


- Logic function defined in the form of a table




# Logic Gates and Networks

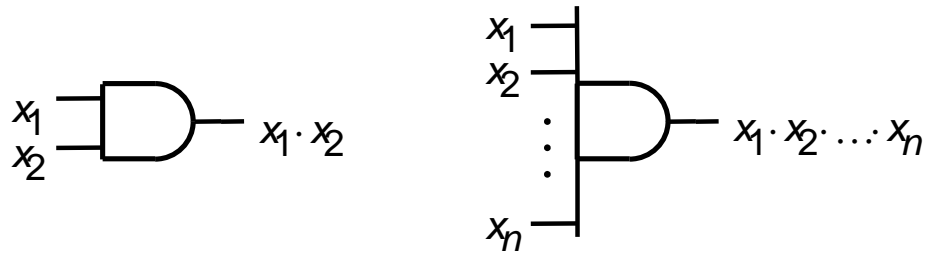

(a) AND gates

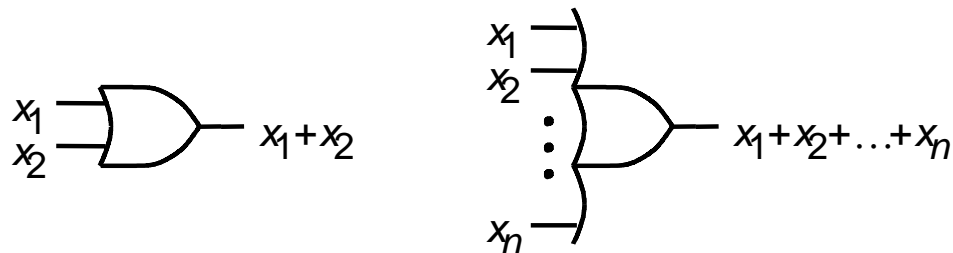


(b) OR gates

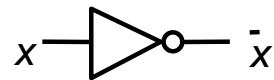


(c) NOT gate

# Logic Analysis & Synthesis

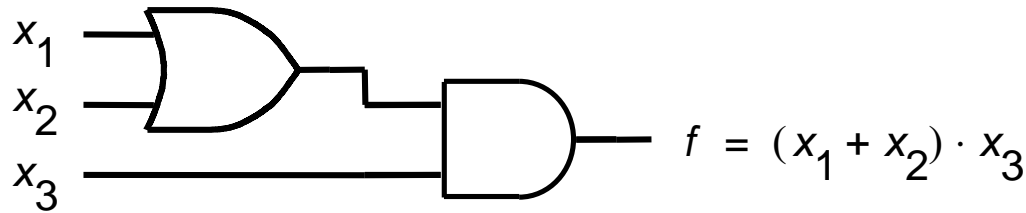

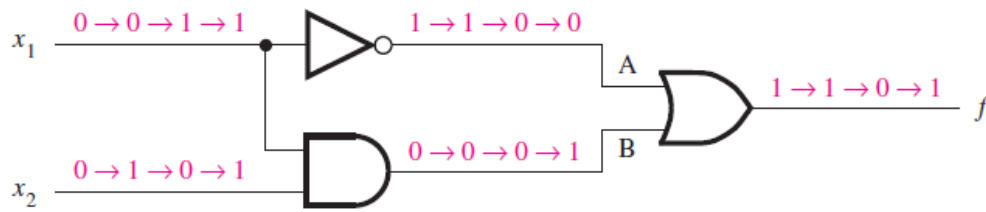- A digital system designer needs:
  - Determine the function performed by a logic network → ***Logic analysis***
  - Designing a new (logic) network that implements a desired function behavior → ***Logic synthesis***




(a) Network that implements  $f = \bar{x}_1 + x_1 \cdot x_2$




$x_1$	$x_2$	$f(x_1, x_2)$	A	B
0	0	1	1	0
0	1	1	1	0
1	0	0	0	0
1	1	1	0	1

(b) Truth table

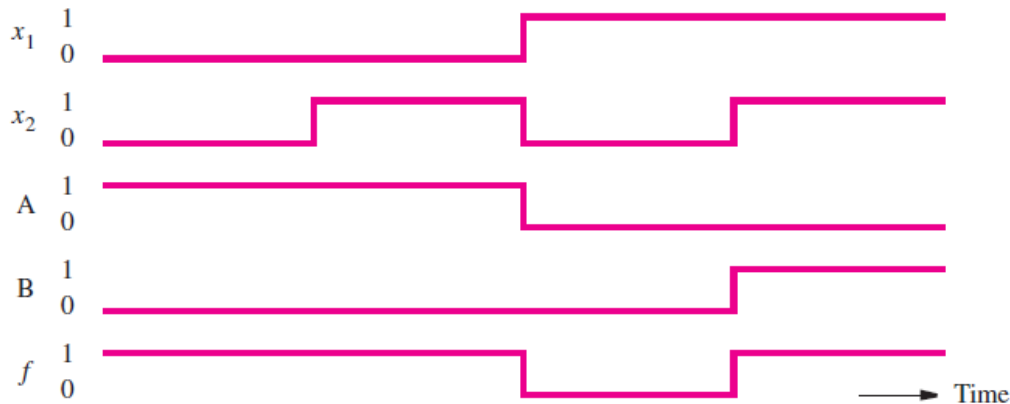

(c) Timing diagram

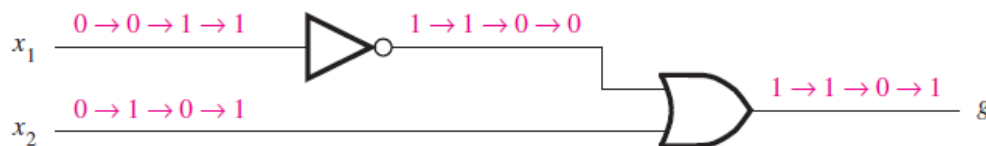

(d) Network that implements  $g = \bar{x}_1 + x_2$

Functionally  
equivalent networks  
→  $f(x_1, x_2)$  and  $g(x_1, x_2)$   
are functionally  
equivalent  
→ It makes sense to  
use the simpler one,  
which is less costly  
to implement

# Boolean Algebra

- In 1849 George Boole published a scheme for the algebraic description of processes involved in logical thoughts and reasoning
- In the late 1930s Claude Shannon showed that Boolean algebra provides an effective means of describing circuits built with switches

# Axioms (Assumptions)

$$1a. \quad 0 \cdot 0 = 0$$

$$1b. \quad 1 + 1 = 1$$

$$2a. \quad 1 \cdot 1 = 1$$

$$2b. \quad 0 + 0 = 0$$

$$3a. \quad 0 \cdot 1 = 1 \cdot 0 = 0$$

$$3b. \quad 1 + 0 = 0 + 1 = 1$$

$$4a. \quad \text{If } x = 0, \text{ then } \bar{x} = 1$$

$$4b. \quad \text{If } x = 1, \text{ then } \bar{x} = 0$$

# Single- Variable Theorem

$$5a. \quad x \cdot 0 = 0$$

$$5b. \quad x + 1 = 1$$

$$6a. \quad x \cdot 1 = x$$

$$6b. \quad x + 0 = x$$

$$7a. \quad x \cdot x = x$$

$$7b. \quad x + x = x$$

$$8a. \quad x \cdot \bar{x} = 0$$

$$8b. \quad x + \bar{x} = 1$$

$$9. \quad \bar{\bar{x}} = x$$

# Properties

10a.  $x \cdot y = y \cdot x$

*Commutative*

10b.  $x + y = y + x$

11a.  $x \cdot (y \cdot z) = (x \cdot y) \cdot z$

*Associative*

11b.  $x + (y + z) = (x + y) + z$

12a.  $x \cdot (y + z) = x \cdot y + x \cdot z$

*Distributive*

12b.  $x + y \cdot z = (x + y) \cdot (x + z)$

13a.  $x + x \cdot y = x$

*Absorption*

13b.  $x \cdot (x + y) = x$

14a.  $x \cdot y + x \cdot \bar{y} = x$

*Combining*

14b.  $(x + y) \cdot (x + \bar{y}) = x$

15a.  $\overline{x \cdot y} = \bar{x} + \bar{y}$

*DeMorgan's theorem*

15b.  $\overline{x + y} = \bar{x} \cdot \bar{y}$

16a.  $x + \bar{x} \cdot y = x + y$

16b.  $x \cdot (\bar{x} + y) = x \cdot y$

17a.  $x \cdot y + y \cdot z + \bar{x} \cdot z = x \cdot y + \bar{x} \cdot z$

*Consensus*

17b.  $(x + y) \cdot (y + z) \cdot (\bar{x} + z) = (x + y) \cdot (\bar{x} + z)$

# More Comments

- Duality
  - Dual of any true statement in Boolean algebra is also a true statement
  - Implying that at least two different ways exist to express every logic function with Boolean algebra; often one expression leads to a simpler physical implementation than the other
- Huntington's basic postulates
  - Theorems 5 and 8 and Properties 10 and 12
  - All the other identities can be derived from these postulates



# More Comments

- OR
  - Logical sum
  - +
- AND
  - Logical product
  - ·
- Operation order
  - NOT  $\rightarrow$  AND  $\rightarrow$  OR
  - To be clear, use parentheses for a complex logic function



# Logic Analysis & Synthesis

$x_1$	$x_2$	$f(x_1, x_2)$
0	0	1
0	1	1
1	0	0
1	1	1

$$f(x_1, x_2) = x_1x_2 + \bar{x}_1\bar{x}_2 + \bar{x}_1x_2$$

- A possible procedure for designing a logic circuit that implements this truth table is to create a product term that has a value of 1 for each valuation for which the output function  $f$  has to be 1. Then we can take a logical sum of these product terms to realize  $f$ .

# Logic Synthesis

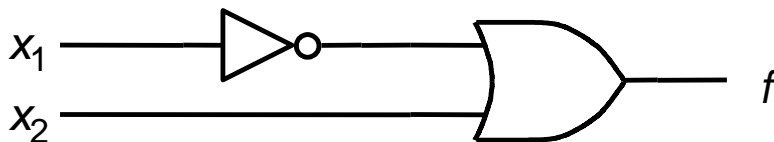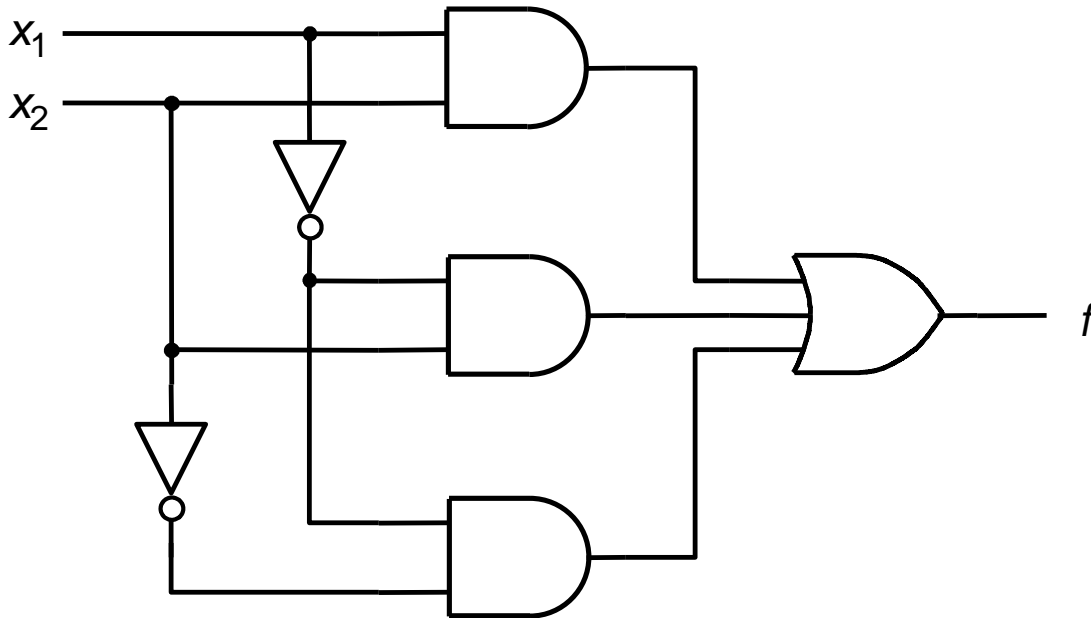

- Not necessarily the optimal in terms of implementation cost (i.e., many logic gates)
- Further simplification using Boolean algebra's theorems and properties

# Sum of Products

Row number	$x_1$	$x_2$	$x_3$	Minterm	Maxterm
0	0	0	0	$m_0 = \overline{x}_1\overline{x}_2\overline{x}_3$	$M_0 = x_1 + x_2 + x_3$
1	0	0	1	$m_1 = \overline{x}_1\overline{x}_2x_3$	$M_1 = x_1 + x_2 + \overline{x}_3$
2	0	1	0	$m_2 = \overline{x}_1x_2\overline{x}_3$	$M_2 = x_1 + \overline{x}_2 + x_3$
3	0	1	1	$m_3 = \overline{x}_1x_2x_3$	$M_3 = x_1 + \overline{x}_2 + \overline{x}_3$
4	1	0	0	$m_4 = x_1\overline{x}_2\overline{x}_3$	$M_4 = \overline{x}_1 + x_2 + x_3$
5	1	0	1	$m_5 = x_1\overline{x}_2x_3$	$M_5 = \overline{x}_1 + x_2 + \overline{x}_3$
6	1	1	0	$m_6 = x_1x_2\overline{x}_3$	$M_6 = \overline{x}_1 + \overline{x}_2 + x_3$
7	1	1	1	$m_7 = x_1x_2x_3$	$M_7 = \overline{x}_1 + \overline{x}_2 + \overline{x}_3$

- Minterms: a product term in which each of the n variables appears once
- Sum of minterms  $\rightarrow$  sum of products
- Maxterms: the complements of minterms

# Sum of Products

Row number	$x_1$	$x_2$	$x_3$	$f(x_1, x_2, x_3)$
0	0	0	0	0
1	0	0	1	1
2	0	1	0	0
3	0	1	1	0
4	1	0	0	1
5	1	0	1	1
6	1	1	0	1
7	1	1	1	0

$$f(x_1, x_2, x_3) = \bar{x}_1\bar{x}_2x_3 + x_1\bar{x}_2\bar{x}_3 + x_1\bar{x}_2x_3 + x_1x_2\bar{x}_3$$

$$f = (\bar{x}_1 + x_1)\bar{x}_2x_3 + x_1(\bar{x}_2 + x_2)\bar{x}_3$$

$$= 1 \cdot \bar{x}_2x_3 + x_1 \cdot 1 \cdot \bar{x}_3$$

$$= \bar{x}_2x_3 + x_1\bar{x}_3$$

$$f(x_1, x_2, x_3) = \sum(m_1, m_4, m_5, m_6)$$

# Product of Sums

Row number	$x_1$	$x_2$	$x_3$	Minterm	Maxterm
0	0	0	0	$m_0 = \overline{x}_1 \overline{x}_2 \overline{x}_3$	$M_0 = x_1 + x_2 + x_3$
1	0	0	1	$m_1 = \overline{x}_1 \overline{x}_2 x_3$	$M_1 = x_1 + x_2 + \overline{x}_3$
2	0	1	0	$m_2 = \overline{x}_1 x_2 \overline{x}_3$	$M_2 = x_1 + \overline{x}_2 + x_3$
3	0	1	1	$m_3 = \overline{x}_1 x_2 x_3$	$M_3 = x_1 + \overline{x}_2 + \overline{x}_3$
4	1	0	0	$m_4 = x_1 \overline{x}_2 \overline{x}_3$	$M_4 = \overline{x}_1 + x_2 + x_3$
5	1	0	1	$m_5 = x_1 \overline{x}_2 x_3$	$M_5 = \overline{x}_1 + x_2 + \overline{x}_3$
6	1	1	0	$m_6 = x_1 x_2 \overline{x}_3$	$M_6 = \overline{x}_1 + \overline{x}_2 + x_3$
7	1	1	1	$m_7 = x_1 x_2 x_3$	$M_7 = \overline{x}_1 + \overline{x}_2 + \overline{x}_3$

- Maxterm: the dual of minterm
- Product of sums: the dual of SoP


# Maxterms; Product of Sums

$$\begin{aligned}\bar{f}(x_1, x_2, x_3) &= m_0 + m_2 + m_3 + m_7 \\ &= \bar{x}_1\bar{x}_2\bar{x}_3 + \bar{x}_1x_2\bar{x}_3 + \bar{x}_1x_2x_3 + x_1x_2x_3\end{aligned}$$


Row number	$x_1$	$x_2$	$x_3$	$f(x_1, x_2, x_3)$
0	0	0	0	0
1	0	0	1	1
2	0	1	0	0
3	0	1	1	0
4	1	0	0	1
5	1	0	1	1
6	1	1	0	1
7	1	1	1	0

$$\begin{aligned}f &= \overline{m_0 + m_2 + m_3 + m_7} \\ &= \bar{m}_0 \cdot \bar{m}_2 \cdot \bar{m}_3 \cdot \bar{m}_7 \\ &= M_0 \cdot M_2 \cdot M_3 \cdot M_7 \\ &= (x_1 + x_2 + x_3)(x_1 + \bar{x}_2 + x_3)(x_1 + \bar{x}_2 + \bar{x}_3)(\bar{x}_1 + \bar{x}_2 + \bar{x}_3) \\ f(x_1, x_2, x_3) &= \Pi(M_0, M_2, M_3, M_7)\end{aligned}$$

# NAND and NOR Networks

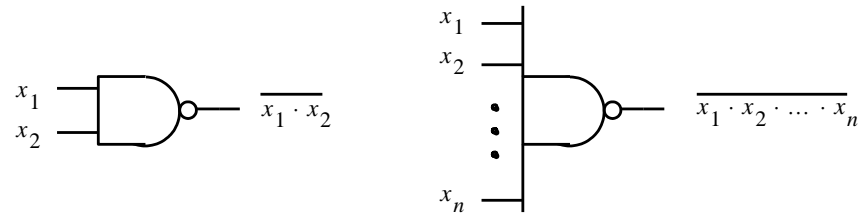

(a) NAND gates

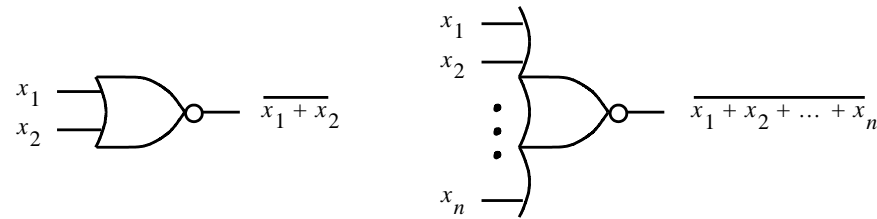


(b) NOR gates


- Considering CMOS implementation technology, NAND and NOR are attractive as they are implemented with simpler electronic circuits than AND and OR



# DeMorgan's Theorem



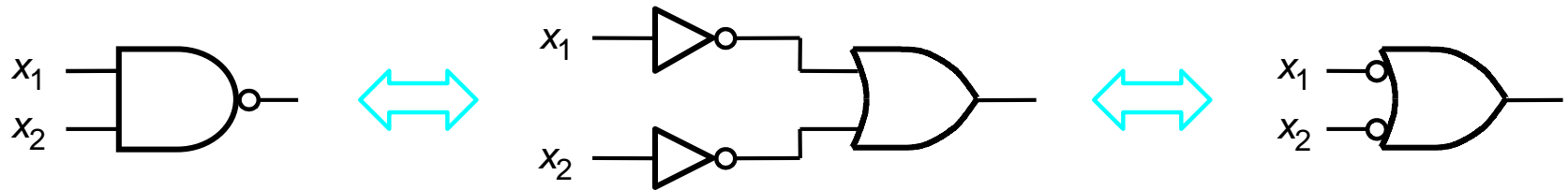

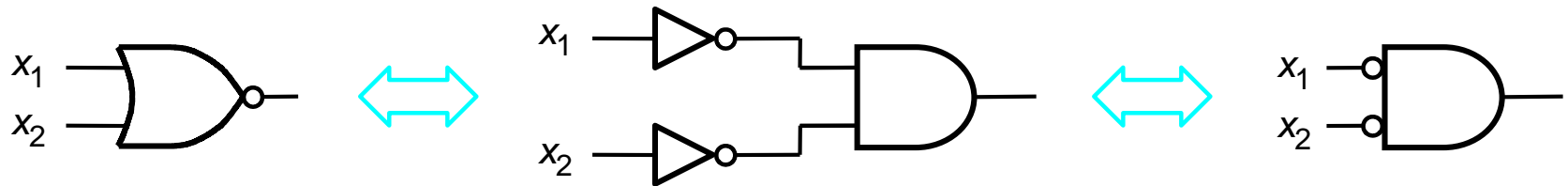
$$(a) \overline{X_1 X_2} = \bar{X}_1 + \bar{X}_2$$




$$(b) \overline{X_1 + X_2} = \bar{X}_1 \bar{X}_2$$


# NAND for a SoP Network

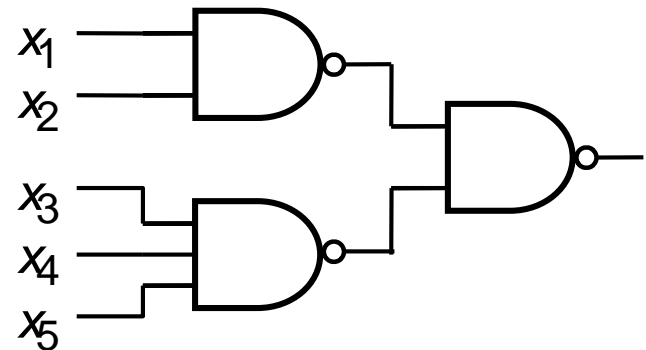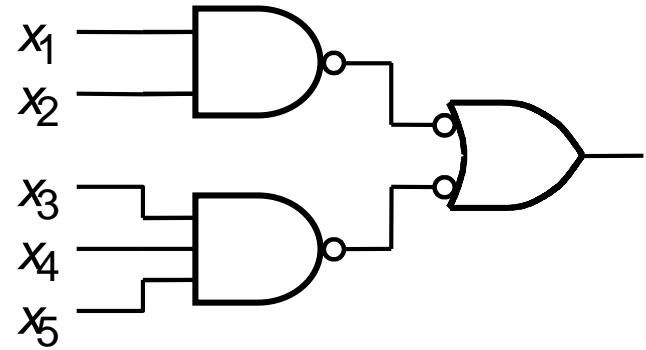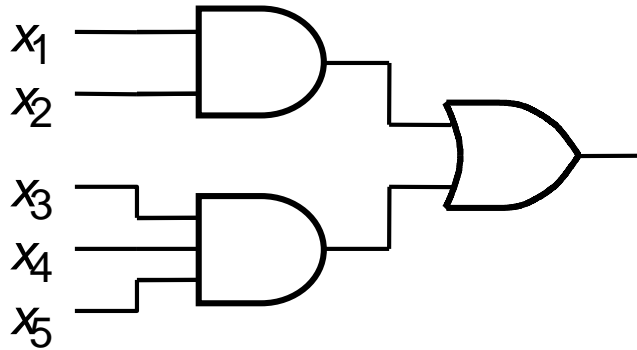

# NOR for a PoS Network

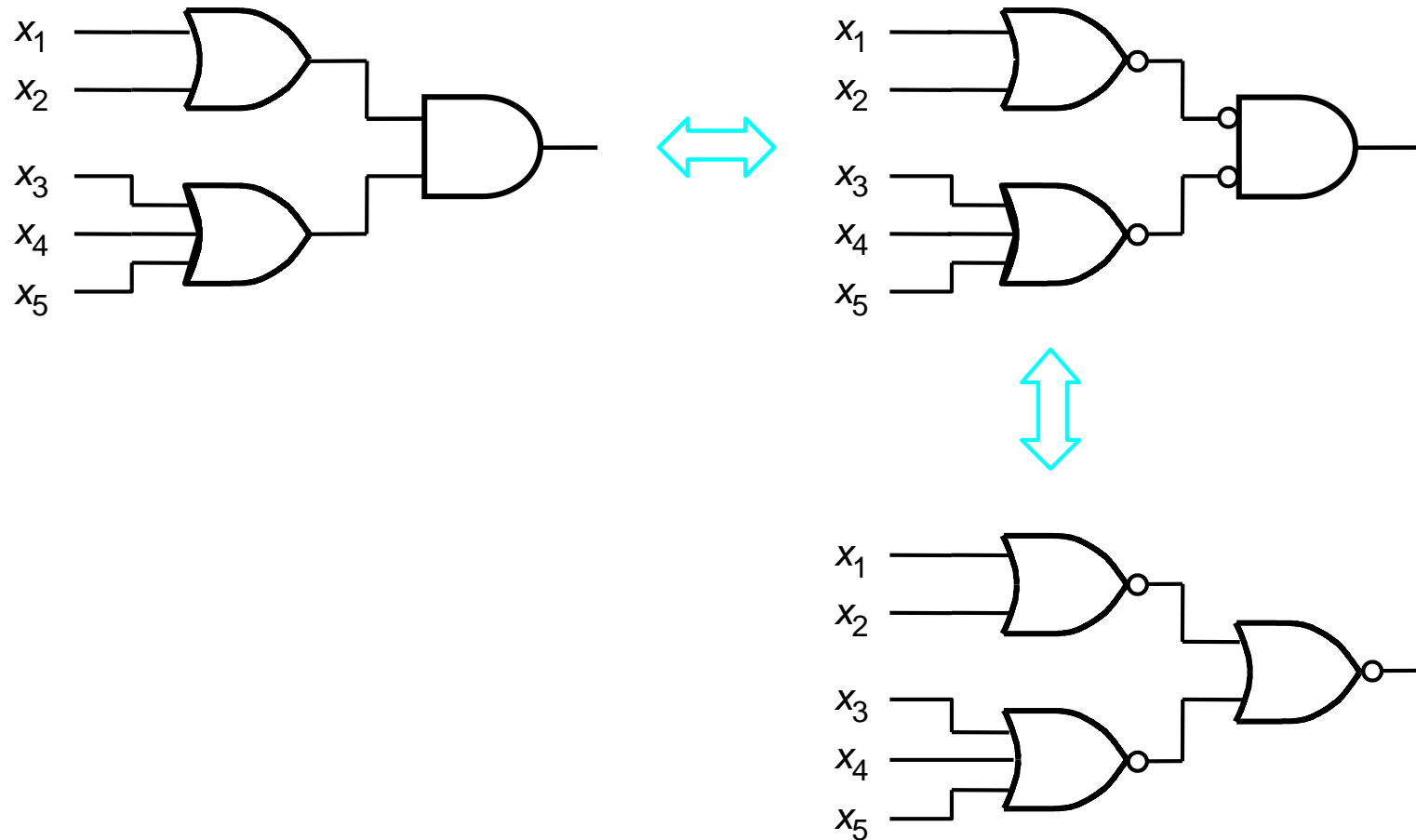

# Number Display Logic Function Example

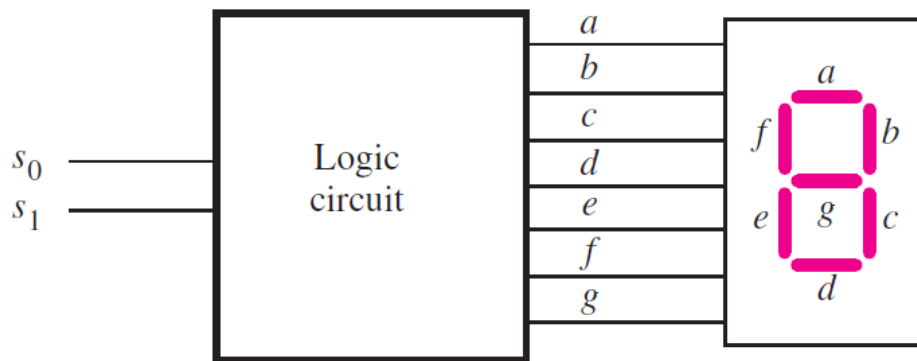

(a) Logic circuit and 7-segment display

	$s_1$	$s_0$	$a$	$b$	$c$	$d$	$e$	$f$	$g$
0	0	0	1	1	1	1	1	1	0
1	0	1	0	1	1	0	0	0	0
2	1	0	1	1	0	1	1	0	1

(b) Truth table

$$a = d = e = \bar{s}_0$$

$$b = 1$$

$$c = \bar{s}_1$$

$$f = \bar{s}_1 \bar{s}_0$$

$$g = s_1 \bar{s}_0$$

# Karnaugh Map: A Method to Minimize Logic Circuits

$x_1$	$x_2$	$x_3$	
0	0	0	$m_0$
0	0	1	$m_1$
0	1	0	$m_2$
0	1	1	$m_3$
1	0	0	$m_4$
1	0	1	$m_5$
1	1	0	$m_6$
1	1	1	$m_7$


(a) Truth table

		$x_1 x_2$			
		00	01	11	10
$x_3$	0	$m_0$	$m_2$	$m_6$	$m_4$
	1	$m_1$	$m_3$	$m_7$	$m_5$

(b) Karnaugh map

# Karnaugh Map: A Method to Minimize Logic Circuits

Row number	$x_1$	$x_2$	$x_3$	$f(x_1, x_2, x_3)$
0	0	0	0	0
1	0	0	1	1
2	0	1	0	0
3	0	1	1	0
4	1	0	0	1
5	1	0	1	1
6	1	1	0	1
7	1	1	1	0

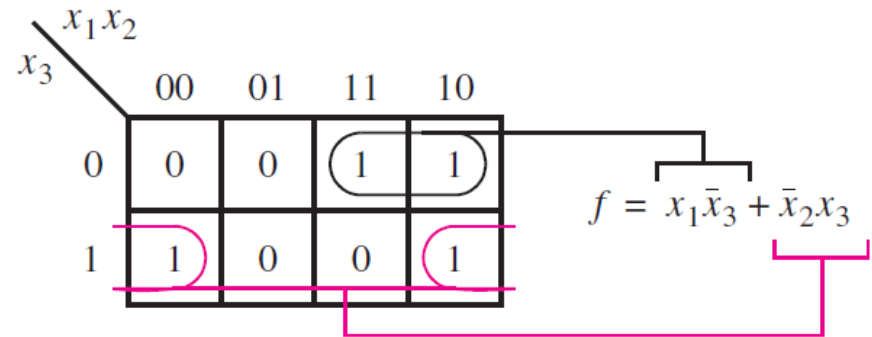

# Incompletely Specified Function

	$x_1x_2$	00	01	11	10
$x_3x_4$	00	0	1	d	0
	01	0	1	d	0
	11	0	0	d	0
	10	1	1	d	1

$$f(x_1, \dots, x_4) = \sum m(2, 4, 5, 6, 10) + D(12, 13, 14, 15)$$

- Certain input conditions can never occur
- We can set the outputs of such input conditions for the given logic function  $f$  to *don't care's* (DCs)
- A logic function definition w/ don't care's

# Strategy for General Logic Minimization

**Literal:** a variable ( $x$ ) or its complement ( $x'$ )

**Product:** an “AND” of literals (e.g.  $xy'z$ ,  $a'bcd'$ )

**Cube:** a product (another equivalent name)

**Minterm:** a product including a literal for every input of the function

*Example:* If a function has 3 inputs,  $A/B/C$ , then  $A'BC'$  is a minterm, but  $A'C$  is not.

A minterm is also an input vector or combination (i.e. corresponds to a single row in the truth table)

**ON-set minterm:** minterm where the function is 1

**OFF-set minterm:** minterm where the function is 0

**DC-set minterm:** minterm where the function is DC (-)

**Implicant:** a cube/product which contains no OFF-set minterm (i.e. 0 value)

**Prime Implicant (PI, prime):** a maximal implicant (i.e. it is contained in no larger implicant); it cannot be combined into another implicant that has fewer literals.

**Essential Prime Implicant (essential):** a prime which contains at least one ON-set minterm (i.e. 1 value) which is not contained by any other prime

**Sum-of-products (SOP, disjunctive normal form):**

a sum of products (“AND-OR” 2-level circuit)

**Cover:** a set of primes (SOP) containing all the ON-set minterms (1 points) of a function

**Complete Sum:** a cover containing all possible prime implicants of the function



# 2-Level Logic Minimization Problem

The 2-Level Logic Minimization Problem: given a Boolean function  $f$

- (i) Find a minimum-cost set of prime implicants which “covers” (i.e. contains) all ON-set minterms -- (... and possibly some DC-set minterms)

Or, equivalently:

- (ii) Find a minimum-cost cover  $F$  of function  $f$

Cost is defined as:

e.g., the number of gates + the total number of inputs to all gates in the circuits. What are the costs of the following functions?

$$f = x_1\bar{x}_2 + x_3\bar{x}_4$$

$$g = (\overline{x_1\bar{x}_2 + x_3})(\bar{x}_4 + x_5)$$

# 2-Level Logic Minimization: Example

		AB			
		00	01	11	10
CD	00	1	1	0	0
	01	0	1	1	0
	11	0	0	1	1
	10	0	0	0	0

# 2-Level Logic Minimization: Example

Solution #1: All Primes = 5 Products (AND gates)

		AB			
		00	01	11	10
CD	00	1	1	0	0
	01	0	1	1	0
	11	0	0	1	1
	10	0	0	0	0

“Complete Sum” = cover containing all prime implicants

# 2-Level Logic Minimization: Example

Solution #2: Subset of Primes = 4 Products (AND gates)

		AB			
		00	01	11	10
CD	00	1	1	0	0
	01	0	1	1	0
	11	0	0	1	1
	10	0	0	0	0

Locally sub-optimal solution

“Redundant Cover” = can remove a product and still have legal cover

# 2-Level Logic Minimization: Example

Solution #3: Subset of Primes = 4 Products (AND gates)

		AB			
		00	01	11	10
CD	00	1	1	0	0
	01	0	1	1	0
	11	0	0	1	1
	10	0	0	0	0

Locally optimal solution

**“Irredundant Cover”** (but still globally sub-optimal!)  
= cannot remove any product and still have legal cover

# 2-Level Logic Minimization: Example

Solution #4: Subset of Primes = 3 Products (AND gates)

		AB			
		00	01	11	10
CD	00	1	1	0	0
	01	0	1	1	0
	11	0	0	1	1
	10	0	0	0	0

Globally optimal solution

OPTIMAL SOLUTION (also irredundant)

# Quine-McCluskey Method

- A systematic method for logic minimization
- Steps
  - Generate all prime implicants for the given function  $f$
  - Find the set of essential prime implicants
  - If the set of essential prime implicants covers all valuations for which  $f=1$ , then this set is the desired cover of  $f$ . Otherwise, determine the nonessential prime implicants that should be added to form a complete minimum-cost cover
- The last step follows heuristic rules and cost comparisons
- [https://en.wikipedia.org/wiki/Quine%E2%80%93McCluskey\\_algorithm](https://en.wikipedia.org/wiki/Quine%E2%80%93McCluskey_algorithm)

# Quine-McCluskey Method: Examples

Example #1:  $f(A,B,C,D) = m(0,4,5,11,15) + d(2,6,9)$

[m = ON-set minterms, d = DC-set minterms]

		AB			
		00	01	11	10
CD	00	1	1	0	0
	01	0	1	0	-
	11	0	0	1	1
	10	-	-	0	0



# Quine-McCluskey Method: Examples

## Example #1 (cont.)

A 4x4 Karnaugh map for variables AB and CD. The columns are labeled AB (00, 01, 11, 10) and the rows are labeled CD (00, 01, 11, 10). The map contains 1s at (00,00), (01,00), (01,01), (11,11), (10,11), and (10,10). Don't care cells (indicated by '-') are at (00,10), (01,10), (11,00), and (10,01). Four prime implicants are circled in pink: P1 is a vertical line covering the first column (CD 00, 01, 11, 10); P2 is a vertical line covering the second column (CD 00, 01); P3 is a horizontal line covering the third and fourth rows (AB 11, 10); and P4 is a horizontal line covering the fourth row (AB 01, 10). Arrows from the labels P1, P2, P3, and P4 point to their respective circled regions.

	AB			
	00	01	11	10
CD 00	1	1	0	0
CD 01	0	1	0	- P4
CD 11	0	0	1	1
CD 10	-	-	0	0

Generate all prime implicants

# Quine-McCluskey Method: Examples

## Example #1 (cont.)

Diagram illustrating the Quine-McCluskey method for Example #1 (cont.). The Karnaugh map shows the function with prime implicants (P1, P2, P3, P4) and distinguished minterms (marked with \*).

	AB			
	00	01	11	10
CD				
00	1 *	1	0	0
01	0	1 *	0	- P4
11	0	0	1 *	1
10	-	-	0	0

Annotations: P1 (grouping 00,01), P2 (grouping 01,11), P3 (grouping 11,10), P4 (grouping 01,10). Distinguished minterms are marked with \*.

\* = distinguished minterm

## Prime Implicant Table

prime implicants

	P1	P2	P3	P4
* 0	X			
4	X	X		
* 5		X		
11			X	X
* 15			X	

○ = essential prime

Approach: remove & save essentials {p1, p2, p3}, and delete intersecting rows ... empty table: nothing left to cover.

# Quine-McCluskey Method: Examples

Example #2:  $f(A,B,C) = m(0,1,2,6) + d(5)$

[m = ON-set minterms, d = DC-set minterms]


		A	
		0	1
BC	00	1	0
	01	1	-
	11	0	0
	10	1	1

More complex example: illustrates  
“table reduction step” using column dominance

# Quine-McCluskey Method: Examples

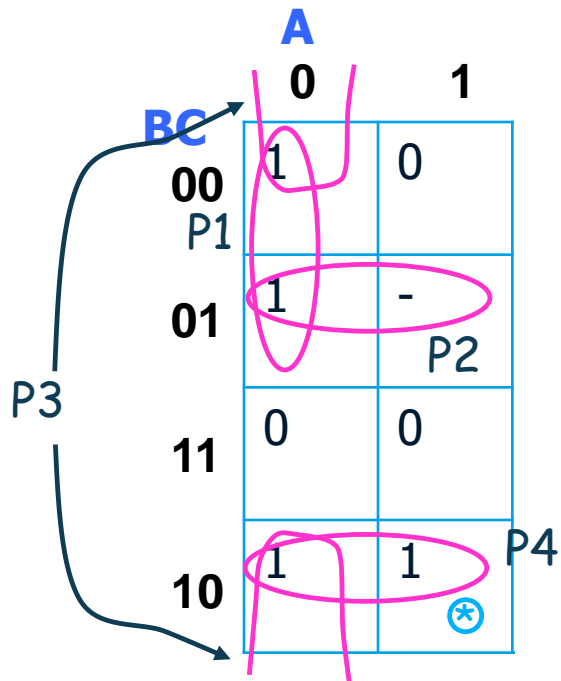Example #2:  $f(A,B,C) = m(0,1,2,6) + d(5)$

[m = ON-set minterms, d = DC-set minterms]



⊛ = distinguished minterm

Prime Implicant Table

prime implicants

	P1	(P2)	P3	P4
0	X		X	
1	X			X
2		X	X	
⊛ 6		X		

ON-set minterms

○ = essential prime

Initial PI Table

# Quine-McCluskey Method: Examples

Example #2:  $f(A,B,C) = m(0,1,2,6) + d(5)$

[m = ON-set minterms, d = DC-set minterms]

		prime implicants			
		P1	(P2)	P3	P4
ON-set minterms	0	X		X	
	1	X			X
	2		X	X	
	*6		X		

○ = essential prime

Initial PI Table

		prime implicants		
		P1	P3	P4
ON-set minterms	0	X	X	
	1	X		X

Reduced PI Table (a)

Approach: remove & save essential p2, and delete intersecting rows.

# Quine-McCluskey Method: Examples

Example #2:  $f(A,B,C) = m(0,1,2,6) + d(5)$

[m = ON-set minterms, d = DC-set minterms]

prime implicants

	P1	P3	P4
0	X	X	
1	X		X

ON-set minterms

Reduced PI Table (a)

prime implicants

	P1
0	X
1	X

Reduced PI Table (b)

“Column Dominance”:

- column p1 ‘column-dominates’ column p3
- column p1 ‘column-dominates’ column p4
- ...delete dominated columns {p3,p4}

# Quine-McCluskey Method: Examples

Example #2:  $f(A,B,C) = m(0,1,2,6) + d(5)$

[m = ON-set minterms, d = DC-set minterms]

prime implicants

	<b>(P1)</b>
0	X
1	X

⊙ = secondary essential prime

“Secondary Essential Primes”:  
- column p1 has now become ‘essential’

Approach: remove & save secondary essential p1,  
and delete intersecting rows.  
... empty table: nothing left to cover.

Reduced PI Table (b)

Final solution: {p1,p2}