

Columbia University
Department of Electrical Engineering
Department of Computer Science
CSEE W4823 Spring 2018
Mid Exam

Name: _____ **UID:** _____

Problem	Full Credit	Your Points
Total	100	

**Note: For full credit, (1) show the pertinent work leading to your answers and
(2) avoid unnecessarily long elaboration on answers.**

1. (10) Find the minimum-cost SOP and POS forms for the function:

$$f(x_1, x_2, x_3, x_4) = \sum m(0, 2, 8, 9, 10, 15) + D(1, 3, 6, 7)$$

2. (10) In a ternary number system there are three digits: 0, 1, and 2. Right figure defines a ternary half-adder. Design a logic circuit that implement this half-adder using binary-encoded signals such that two bits are used for each ternary digit. Let $A=a_1a_0$, $B=b_1b_0$, and $\text{Sum}=s_1s_0$; note that Carry is just a binary signal. Use the following encoding: $00=(0)_3$, $01=(1)_3$, and $10=(2)_3$. Minimize the cost of the circuit.

AB	Carry	Sum
00	0	0
01	0	1
02	0	2
10	0	1
11	0	2
12	1	0
20	0	2
21	1	0
22	1	1

3. (20) Design a 4-b shift register that shifts 1 bit per clock cycle. Use *latch* and other logic circuits. Derive two different circuit diagrams.

4. (10) Given a 100-MHz clock signal, derive a circuit using D flip-flops to generate 50-MHz and 25-MHz clock signals. Draw a timing diagram for all three clock signals, assuming reasonable delays.

5. (10) Write a Verilog code that represents a T flip-flop with an asynchronous clear input. Use behavior code, rather than structural code.


6. (15) Draw the logic circuit diagram represented by the code below. What is its counting sequence?

```
module lfsr (R, L, Clock, Q);  
  input  [0:2] R;  
  input  L, Clock;  
  output reg [0:2] Q;  
  
  always @(posedge Clock)  
    if (L)  
      Q <= R;  
    else  
      begin  
        Q[0] = Q[2];  
        Q[1] = Q[0];  
        Q[2] = Q[1] ^ Q[2];  
      end  
endmodule
```


7. (10) Transform the following single-precision floating point number into decimal and hexadecimal number.

10100011101010111011101000111011

 8. (15) Assume that a gate array contains the type of logic cell depicted in the figure below. The inputs in_1, \dots, in_7 can be connected to either 1 or 0, or to any logic signal.



- (a) Show how the logic cell can be used to realize $f = x_1x_2 + x_3$
- (b) Show how the logic cell can be used to realize $f = x_1x_3 + x_2x_3$

