



**DO NOT SHARE  
SLIDES AND CLASS MATERIALS  
ON ONLINE SITES**

Course Home

# Advanced Logic Design

## Testing

Mingoo Seok  
Columbia University

BV chapters: 11

# Testing

- You designed a logic circuit. Then you need to test it working to the logic specification
- The logic circuit is very large and it is not trivial to test them in a short amount of time (longer testing time increases manufacturing cost)
- Testing sequential circuits is even more complex than combinational counterparts due to the state dependencies


# Fault Model

- Stuck-At model
  - Stuck-at-0
  - Stuck-at-1
  - Node  $w$  is stuck-at-0:  $w/0$
  - Node  $w$  is stuck-at-1:  $w/1$
- Physical meaning
  - Short to power supply voltage or ground
  - Open
  - Drain current is too small

# Test Set

- The goal is to create several *tests* that are able to detect the occurrence of one or more faults
- *Test set*: a complete set of tests for a given circuit

# Test Set Example

 


Test $w_1 w_2 w_3$	Fault detected									
	$a/0$	$a/1$	$b/0$	$b/1$	$c/0$	$c/1$	$d/0$	$d/1$	$f/0$	$f/1$
000		✓						✓		✓
001		✓		✓				✓		✓
010		✓				✓		✓		✓
011			✓		✓		✓		✓	
100	✓								✓	
101	✓								✓	
110	✓								✓	
111									✓	

Test set = {001, 010, 011, 100}

# Test Set

- Instead of  $2^n$  test, a smaller number of tests can detect all the faults of interest (stuck-at-1 and stuck-at-0 faults)
- In the previous example: 4 out of 8
- Still, inspecting all the nodes of a circuit can take too much time due to the large number of nodes
- How can we do it better?


# Path Sensitizing

 

- Rather than nodes, we can inspect paths
- We can activate (sensitize) a path by ensuring that other paths in the circuits do not determine the value of the output  $f$
- By assigning  $w_2$ ,  $w_3$ , and  $w_4$ , we can make the path  $(a \rightarrow b \rightarrow c \rightarrow f)$  sensitized to input  $w_1$




# Path Sensitizing: Example

 


Test set = {0110, 1100, 1000, 0010, 0x00, 0x01}

# Detecting a Specific Fault

 


- How to check if the node  $b$  is stuck-at-1?
- *Sensitize* the path  $b$ - $d$ - $f$
- *Find the primary input(s)* that makes the node  $b$  to 0
- *Find the other primary input(s)* that have not been set
- $w_1 w_2 w_3 w_4 = 0110$


# Propagating a Fault

 

 - Test if  $b/0$
- D: a stuck-at-0
- Consistency check: if we can apply appropriate values to the primary input variables for propagating a fault




# Propagating a Fault

 

- Let's test if **g/1**
- Propagate via only one NAND will fail the consistency check
- Propagating via both NANDs results in a test vector  $w_1w_2w_3w_4=0000$

# Random Test

$w_1 w_2$	$f_0$	$f_1$	$f_2$	$f_3$	$f_4$	$f_5$	$f_6$	$f_7$	$f_8$	$f_9$	$f_{10}$	$f_{11}$	$f_{12}$	$f_{13}$	$f_{14}$	$f_{15}$
00	0	0	0	0	0	0	0	0	1	1	1	1	1	1	1	1
01	0	0	0	0	1	1	1	1	0	0	0	0	1	1	1	1
10	0	0	1	1	0	0	1	1	0	0	1	1	0	0	1	1
11	0	1	0	1	0	1	0	1	0	1	0	1	0	1	0	1

 


XOR function

# Random Test

- For an  $n$ -variable input function, there are  $2^{2^n}$  possibilities
- 2 input: 16 functions

# Random Test

 

- With each fault,  $f$  becomes one of the ten functions ( $f_5, f_{10}, \dots$ )
- If I use  $w_1 w_2 = 01$ , I can detect  $f_0, f_2, f_3$ , and  $f_{10}$
- $11 \rightarrow f_5, f_7$  and  $f_{15}$
- $10 \rightarrow f_4$  and  $f_{12}$
- **Looks quite effective!**

Fault	Circuit implements
$b/0$	$f_5 = w_2$
$b/1$	$f_{10} = \overline{w_2}$
$c/0$	$f_3 = w_1$
$c/1$	$f_{12} = \overline{w_1}$
$d/0$	$f_0 = 0$
$d/1$	$f_7 = w_1 + w_2$
$h/0$	$f_{15} = 1$
$h/1$	$f_4 = \overline{w_1} w_2$
$k/0$	$f_{15} = 1$
$k/1$	$f_2 = w_1 \overline{w_2}$

# Random Test Coverage

$w_1 w_2$	$f_0$	$f_1$	$f_2$	$f_3$	$f_4$	$f_5$	$f_6$	$f_7$	$f_8$	$f_9$	$f_{10}$	$f_{11}$	$f_{12}$	$f_{13}$	$f_{14}$	$f_{15}$
00	0	0	0	0	0	0	0	0	1	1	1	1	1	1	1	1
01	0	0	0	0	1	1	1	1	0	0	0	0	1	1	1	1
10	0	0	1	1	0	0	1	1	0	0	1	1	0	0	1	1
11	0	1	0	1	0	1	0	1	0	1	0	1	0	1	0	1

- Each test would rule out the faulty functions whose outputs are different from the correct function
- If I choose 01, the correct circuit produces 1; the faulty eight functions producing 0, i.e.,  $f_0, f_1, f_2, f_3, f_8, f_9, f_{10}, f_{11}$ , should be ruled out




# Random Test Coverage

Prob that each faulty circuit can be detected by the first test set


$$P_1 = \frac{1}{2^{2^2} - 1} \cdot 2^{2^2 - 1} = \frac{8}{15} = 0.53$$

Probably that a faulty circuit will be detected by the first m tests

 
$$P_m = \frac{1}{2^{2^n} - 1} \cdot \sum_{i=1}^m 2^{2^n - i}$$



# Sequential Circuit Testing

 

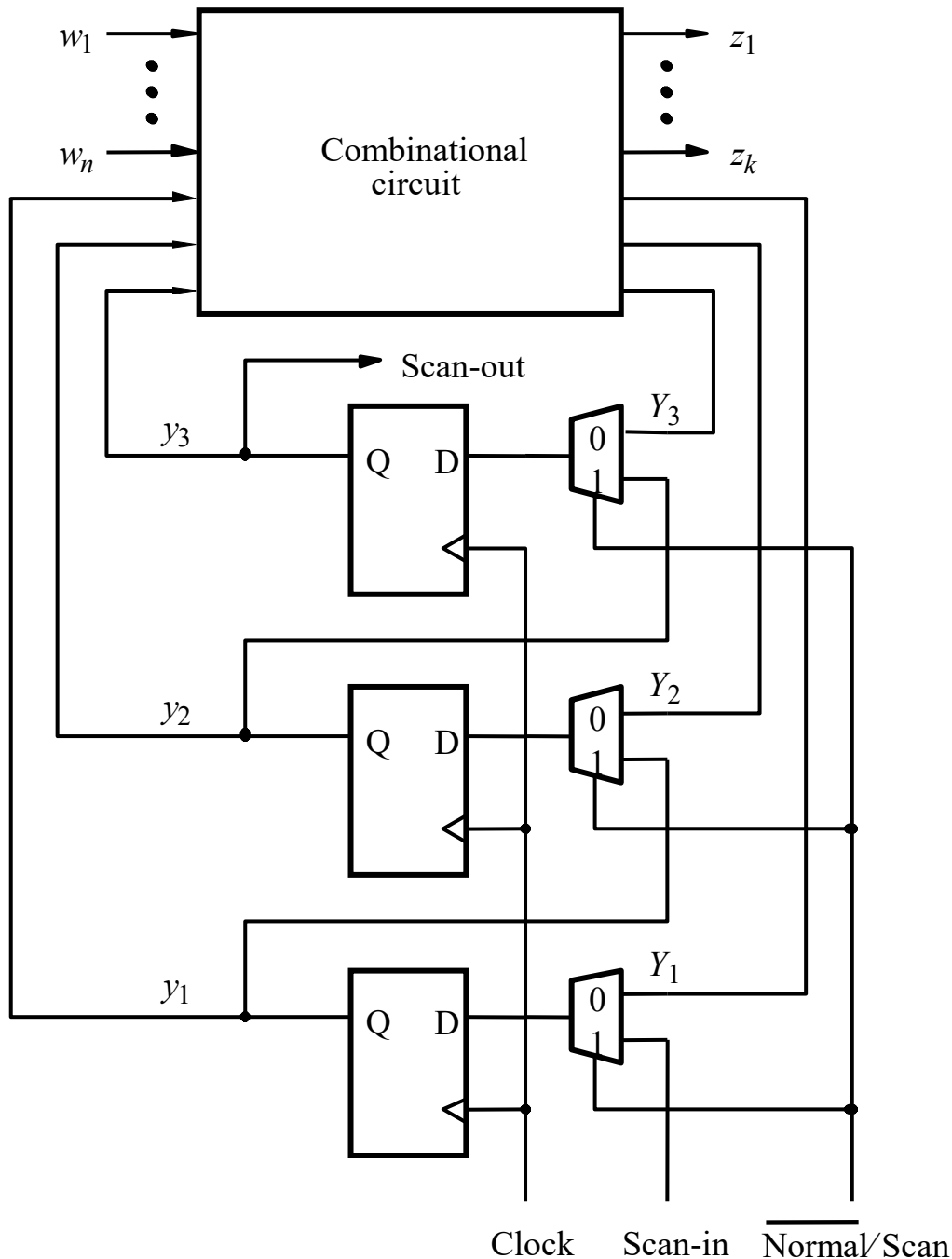- Testing a sequential circuit is much difficult
  - Function is now dependent on states as well
  - It is hard to monitor and assert states because we usually don't have direct access (pins)




# Scan Path

- Add Muxes to the inputs of flip-flops such that the flip-flops can be converted into a shift register

# Scan Path


- Typical testing sequences
  1. Operation of flip-flops are tested
  2. Combinational circuit is tested
  3. Set a state and test the state transitions
- The scan path can't effectively handle if an asynchronous reset/set feature is used during normal operation
- Better to use synchronous set/reset

# Built-In Self-Test

 


- Incorporate the testing capability within the circuit itself so that no external equipment is needed
- Avoid slow and noisy off-chip communication

# PRBSG

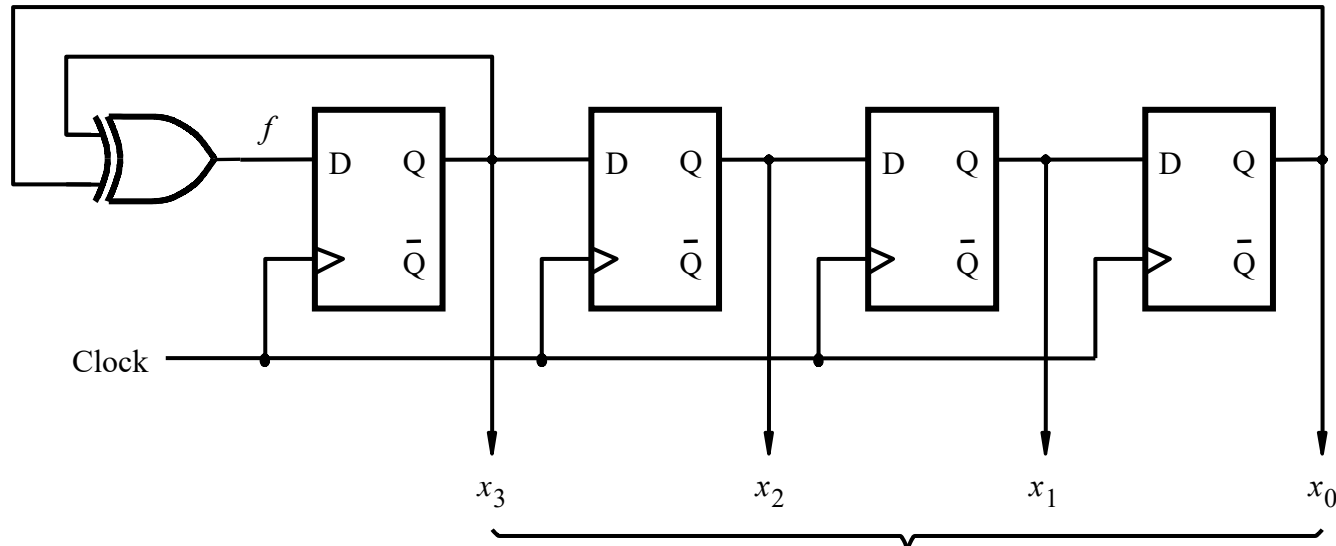


- Pseudorandom binary sequence generator
- Linear feedback shift register: can generate  $2^n - 1$  patterns

# SIC

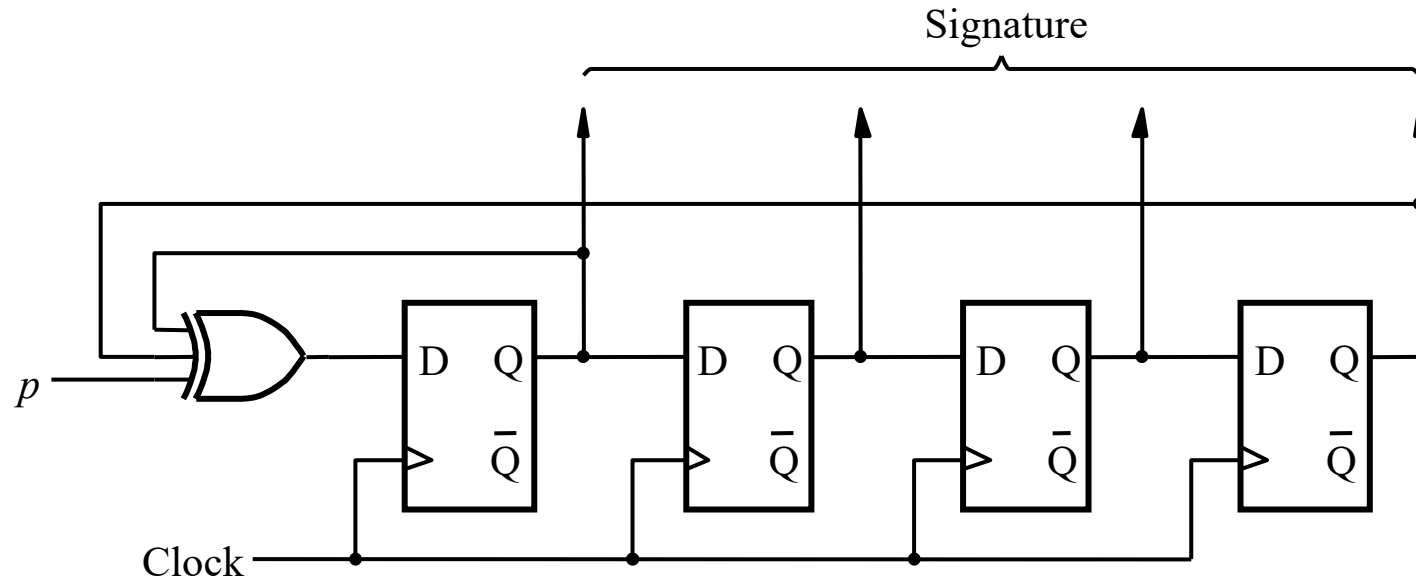

- Single input compressor
- Compress a sequence of patterns into a signature
- A change of one pattern creates different signature


# MIC

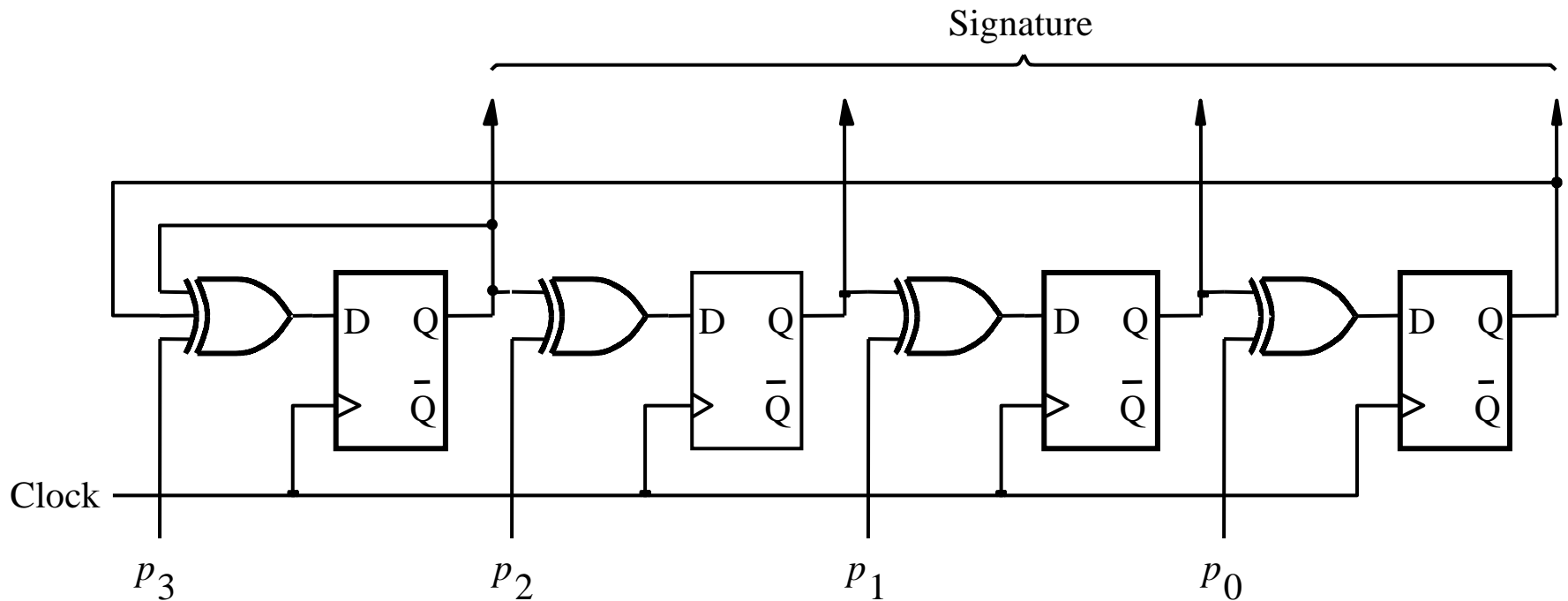


- Multiple input compressor
- Compress a sequence of multi-bit patterns into a signature



# BIST Architecture

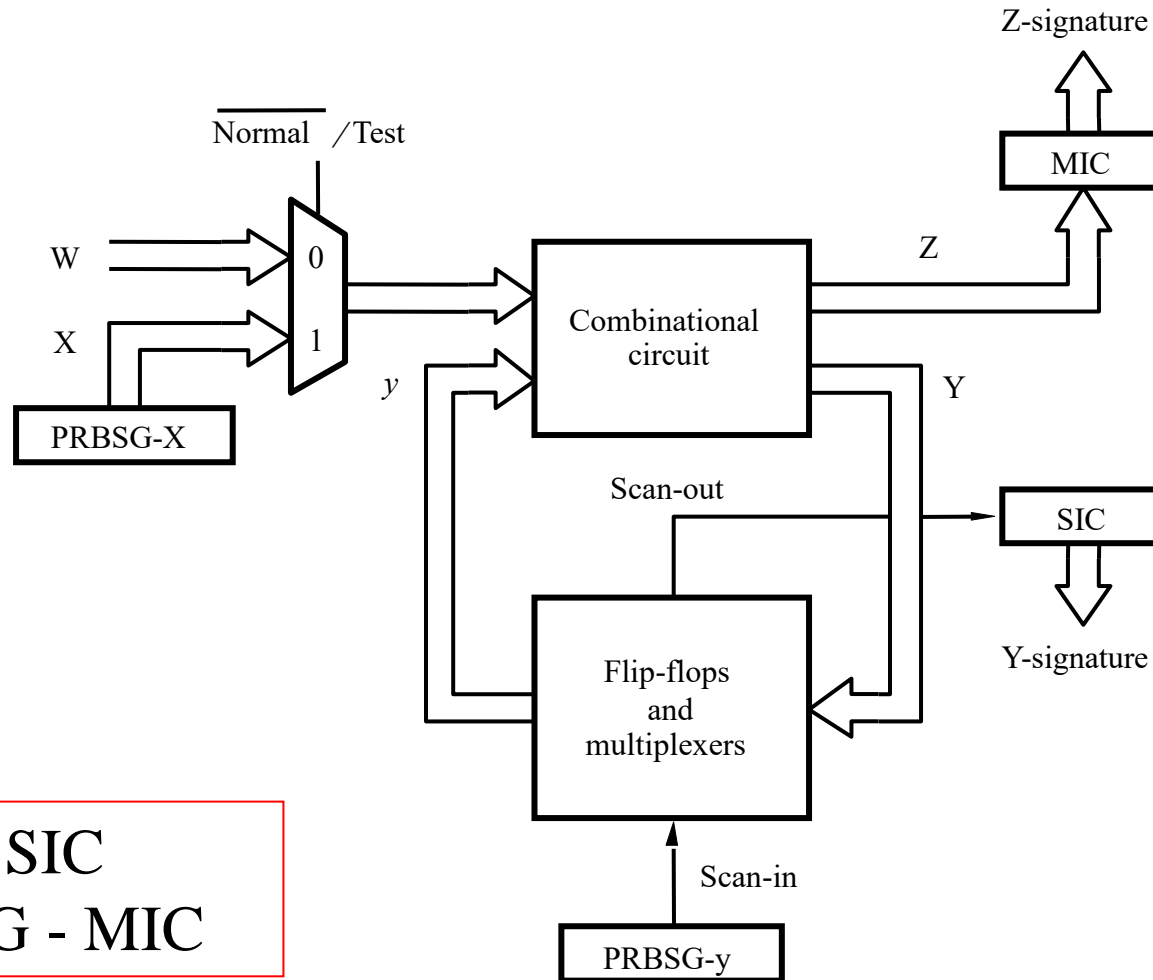


# BILBO

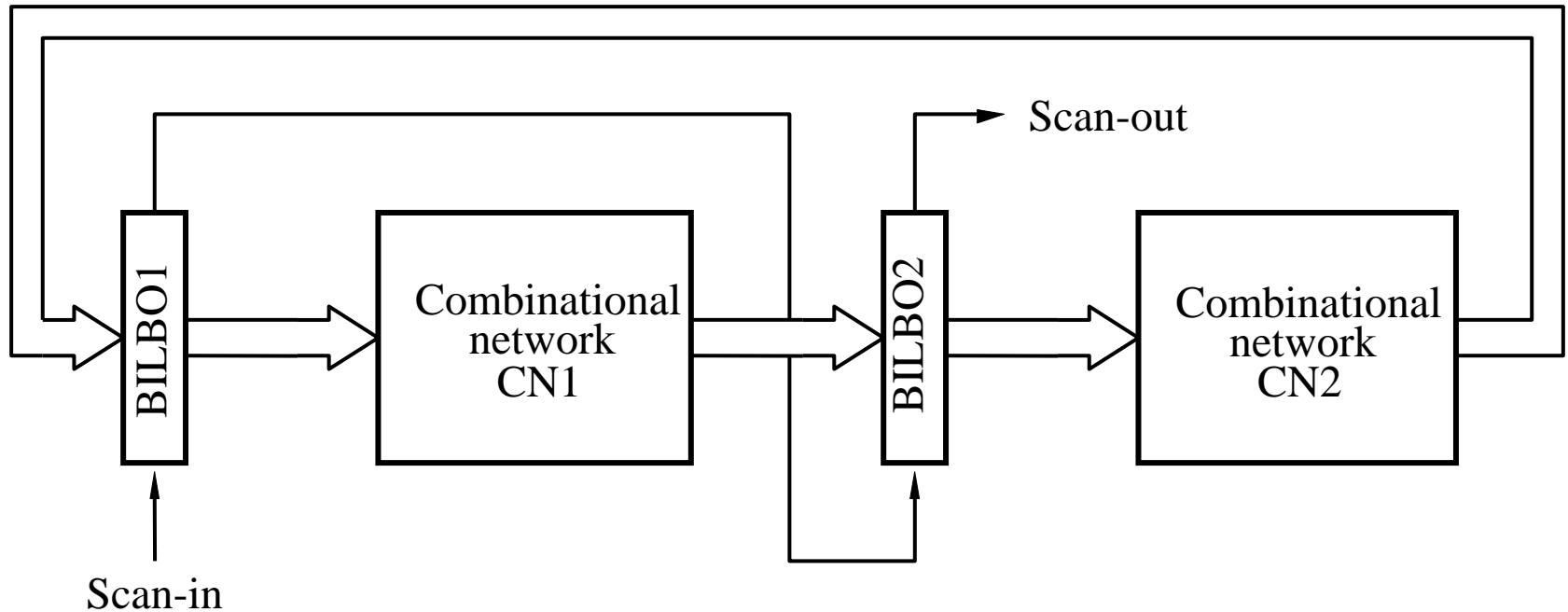

- Built-in Logic Block Observer (BILBO)
- BILBO can be configured to PRBSG, MIC, or regular registers

# BILBO

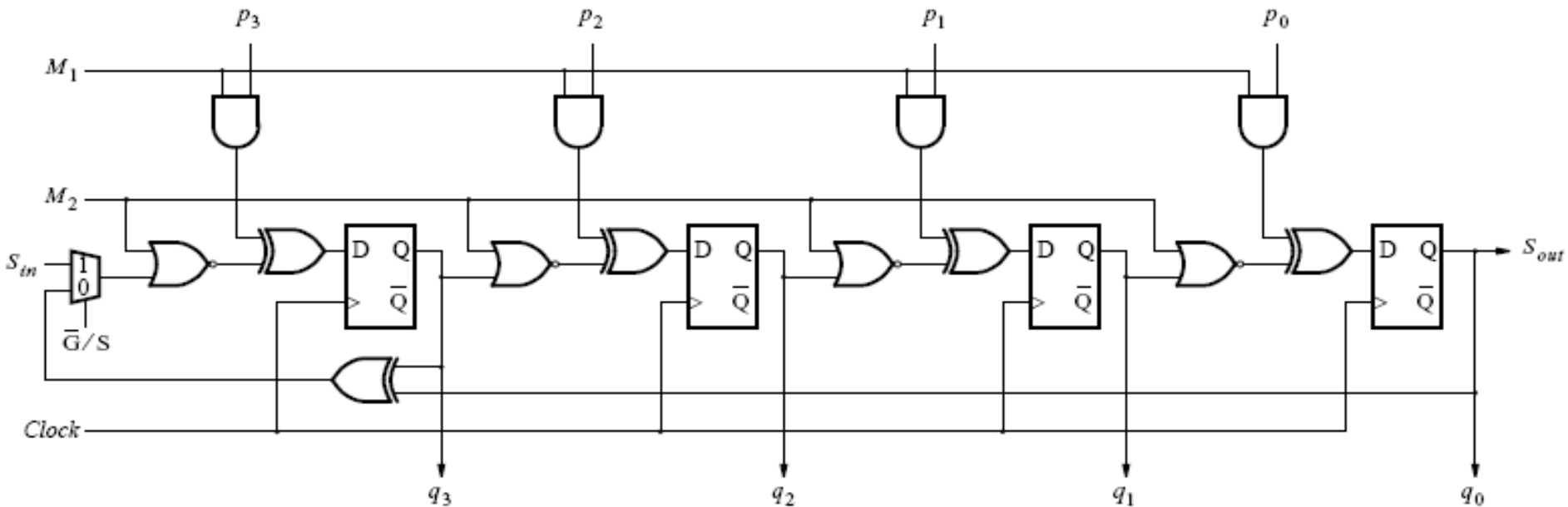

- $M_1M_2=11$ : normal
- 00: shift register mode; if  $\bar{G}/S=0$ , it acts like PRBS
- 10: signature mode
- 01: reset mode

# Boundary Scan

- Chips are soldered onto a printed circuit board, it often becomes impossible to physically attach test probes to such pins
- The scan path concept is extended so that we can scan-in / -out to the primary inputs and outputs of a chip
- Assume each primary input/output is clocked (i.e., registered)
- IEEE Standard 1149.1 for the protocol

# Printed Circuit Board Testing

- Crosstalk
- Power supply noise
- Reflections and terminations
- Power-up
- Functional test
- Timing
- Reliability