



**DO NOT SHARE
SLIDES AND CLASS MATERIALS
ON ONLINE SITES**

Course Home

Advanced Logic Design

Finite State Machine


Mingoo Seok
Columbia University

BV: Secs. 6.1-6.3, 6.5, 6.7

Sequential Circuits (aka FSM)

- In a combinational circuit, the values of the outputs are determined solely by the present values of its inputs
- In a sequential circuit, the values of the outputs depend on the past behavior of the circuit, as well as the present values of its inputs
- A sequential circuit has states, which in conjunction with the present values of inputs determine its behavior.
- Sequential circuits can be:
 - Synchronous – where flip-flops are used to implement the states, and a clock signal is used to control the operation
 - Asynchronous – where no clock is used
- Sequential circuit is formally called a finite state machine (FSM) since it has a finite number of states
- It controls the operation (sequencing) of digital circuits

General Form of a Sync. FSM

 


- w/o the blue line: Moore FSM
- w/ the blue line: Mealy FSM.

FSM Design

Clockcycle:	t ₀	t ₁	t ₂	t ₃	t ₄	t ₅	t ₆	t ₇	t ₈	t ₉	t ₁₀
w:	0	1	0	1	1	0	1	1	1	0	1
z:	0	0	0	0	0	1	0	0	1	1	0


- Example: consider an application where the speed of an automatically-controlled vehicle has to be regulated
 - Input w is 1 if the speed is higher than the target; 0 otherwise
 - The output z is equal to 1 if during two immediately preceding clock cycles the input w was equal to 1; 0 otherwise.
 - Output z is 1 to decelerate
 - All changes in the logic circuit occur on the positive edge of the clock signal

FSM Design

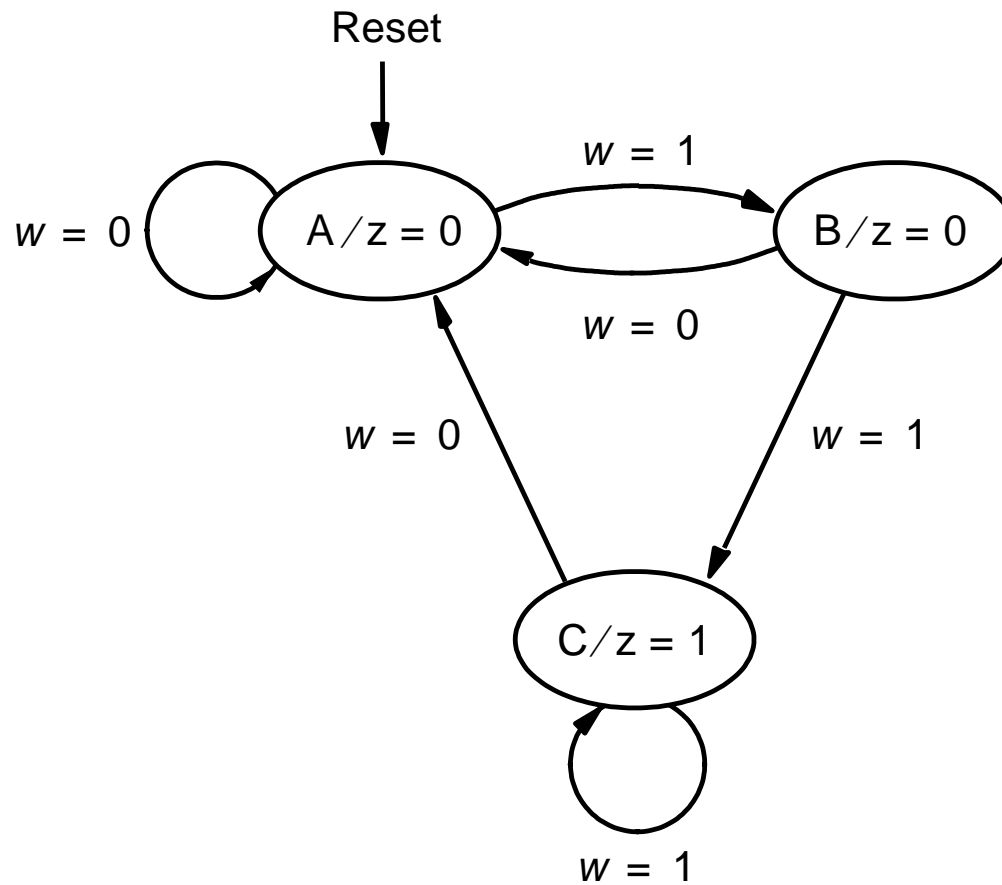

State Table

Present state	Next state		Output z
	$w = 0$	$w = 1$	
A	A	B	0
B	A	C	0
C	A	C	1

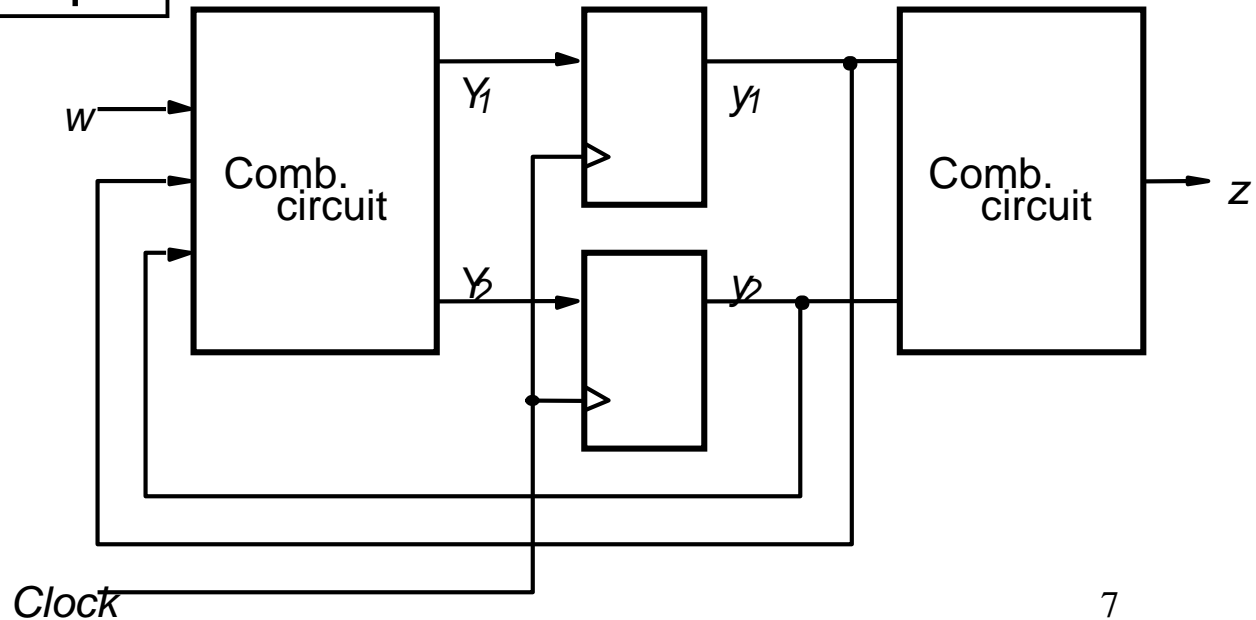

State Table

Present state	Next state		Output z
	$w = 0$	$w = 1$	
A	A	B	0
B	A	C	0
C	A	C	1

	Present state	Next state		Output z
		$w = 0$	$w = 1$	
	$y_2 y_1$	$Y_2 Y_1$	$Y_2 Y_1$	
A	00	00	01	0
B	01	00	10	0
C	10	00	10	1
	11	dd	dd	d

Logic Synthesis

		$y_2 y_1$			
		00	01	11	10
w	0	0	0	d	0
	1	1	0	d	0

Ignoring don't cares

$$Y_1 = w\bar{y}_1\bar{y}_2$$

Using don't cares

$$Y_1 = w\bar{y}_1\bar{y}_2$$

		$y_2 y_1$			
		00	01	11	10
w	0	0	0	d	0
	1	0	1	d	1

$$Y_2 = wy_1\bar{y}_2 + w\bar{y}_1y_2$$


$$\begin{aligned} Y_2 &= wy_1 + wy_2 \\ &= w(y_1 + y_2) \end{aligned}$$

		y_2		y_1	
		0	1		
y_2	0	0	0		
	1	1	d		

$$z = \bar{y}_1y_2$$

$$z = y_2$$



Logic Synthesis

 

Summary of Design Steps

1. Obtain the specification of the desired circuit.
2. Derive a state diagram.
3. Derive the corresponding state table.
4. Reduce the number of states if possible.
5. Decide on the number of state variables.
6. Choose the type of flip-flops to be used.
7. Derive the logic expressions needed to implement the circuit.

Moore to Mealy

  


State Table

Present state	Next state		Output z	
	$w = 0$	$w = 1$	$w = 0$	$w = 1$
A	A	B	0	0
B	A	B	0	1

	Present state	Next state		Output	
		$w = 0$	$w = 1$	$w = 0$	$w = 1$
	y	Y	Y	z	z
A	0	0	1	0	0
B	1	0	1	0	1

Logic Synthesis

 

- Significantly simpler than the Moore implementation
- Faster
- A bit more complex to analyze

Better State Assignment

	Present state y_2y_1	Next state		Output z
		$w = 0$	$w = 1$	
		Y_2Y_1	Y_2Y_1	
A	00	00	01	0
B	01	00	10	0
C	10	00	10	1
	11	dd	dd	d

$$Y_1 = w\bar{y}_1\bar{y}_2$$

$$Y_2 = w(y_1 + y_2)$$

$$z = y_2$$


	Present state y_2y_1	Next state		Output z
		$w = 0$	$w = 1$	
		Y_2Y_1	Y_2Y_1	
A	00	00	01	0
B	01	00	11	0
C	11	00	11	1
	10	dd	dd	d

$$Y_1 = D_1 = w$$


$$Y_2 = D_2 = wy_1$$

$$z = y_2$$

Better State Assignment

 

FSM Optimization

 

- The smaller # of states reduces # of flip-flops, logic circuits complexity, and delay
- S_0 and S_2 are equivalent
 - Same outputs
 - Same state transitions
- Row matching method
- Implication chart method


Row Matching Method

$X = 0010\ 0110\ 1100\ 1010\ 0011\ \dots$

$Z = 0000\ 0001\ 0000\ 0001\ 0000\ \dots$

- Input X and Output Z
- Output is asserted if each 4-bit input sequence is either 0110 or 1010
- Row matching method: quick but not the optimum

Row Matching Method

 

Row Matching Method

Input Sequence	Present State	Next State		Output	
		X=0	X=1	X=0	X=1
Reset	S_0	S_1	S_2	0	0
0	S_1	S_3	S_4	0	0
1	S_2	S_5	S_6	0	0
00	S_3	S_7	S_8	0	0
01	S_4	S_9	S_{10}	0	0
10	S_5	S_{11}	S_{12}	0	0
11	S_6	S_{13}	S_{14}	0	0
000	S_7	S_0	S_0	0	0
001	S_8	S_0	S_0	0	0
010	S_9	S_0	S_0	0	0
011	S_{10}	S_0	S_0	1	0
100	S_{11}	S_0	S_0	0	0
101	S_{12}	S_0	S_0	1	0
110	S_{13}	S_0	S_0	0	0
111	S_{14}	S_0	S_0	0	0

Input Sequence	Present State	Next State		Output	
		X=0	X=1	X=0	X=1
Reset	S_0	S_1	S_2	0	0
0	S_1	S_3	S_4	0	0
1	S_2	S_5	S_6	0	0
00	S_3	S_7	S_8	0	0
01	S_4	S_9	S_{10}	0	0
10	S_5	S_{11}	S_{10}	0	0
11	S_6	S_{13}	S_{14}	0	0
000	S_7	S_0	S_0	0	0
001	S_8	S_0	S_0	0	0
010	S_9	S_0	S_0	0	0
011 or 101	S_{10}	S_0	S_0	1	0
100	S_{11}	S_0	S_0	0	0
110	S_{13}	S_0	S_0	0	0
111	S_{14}	S_0	S_0	0	0

Row Matching Method

Input Sequence	Present State	Next State		Output	
		X=0	X=1	X=0	X=1
Reset	S_0	S_1	S_2	0	0
0	S_1	S_3	S_4	0	0
1	S_2	S_5	S_6	0	0
	00	S_3	S_7	0	0
	01	S_4	S_7	0	0
	10	S_5	S_{10}	0	0
	11	S_6	S_7	0	0
not (011 or 101)	S_7	S_0	S_0	0	0
011 or 101	S_{10}	S_0	S_0	1	0


Input Sequence	Present State	Next State		Output	
		X=0	X=1	X=0	X=1
Reset	S_0	S_1	S_2	0	0
0	S_1	S_3	S_4	0	0
1	S_2	S_4	S_3	0	0
00 or 11	S_3	S_7	S_7	0	0
01 or 10	S_4	S_7	S_{10}	0	0
not (011 or 101)	S_7	S_0	S_0	0	0
011 or 101	S_{10}	S_0	S_0	1	0

Implication Chart Method


Input Sequence	Present State	Next State		Output	
		X=0	X=1	X=0	X=1
Reset	S_0	S_1	S_2	0	0
0	S_1	S_3	S_4	0	0
1	S_2	S_5	S_6	0	0
00	S_3	S_0	S_0	0	0
01	S_4	S_0	S_0	1	0
10	S_5	S_0	S_0	0	0
11	S_6	S_0	S_0	1	0

- 3-bit sequence detector that will output a 1 whenever the machine has observed the serial sequence 010 or 110 at the inputs

Implication Chart Method

 

 Write the possible
equivalent state pairs in
each slot




Eliminate the slots that have
been proved definitely not
equivalent

Implication Chart Method

Input Sequence	Present State	Next State		Output	
		X=0	X=1	X=0	X=1
Reset	S_0	S'_1	S'_1	0	0
0 or 1	S'_1	S'_3	S'_4	0	0
00 or 10	S'_3	S_0	S_0	0	0
01 or 11	S'_4	S_0	S_0	1	0

- State # reduces from 7 to 4
- 3 flip-flops to 2 flip-flops
- Associated logic reduction

Counter as an FSM: Modulo-8 Counter

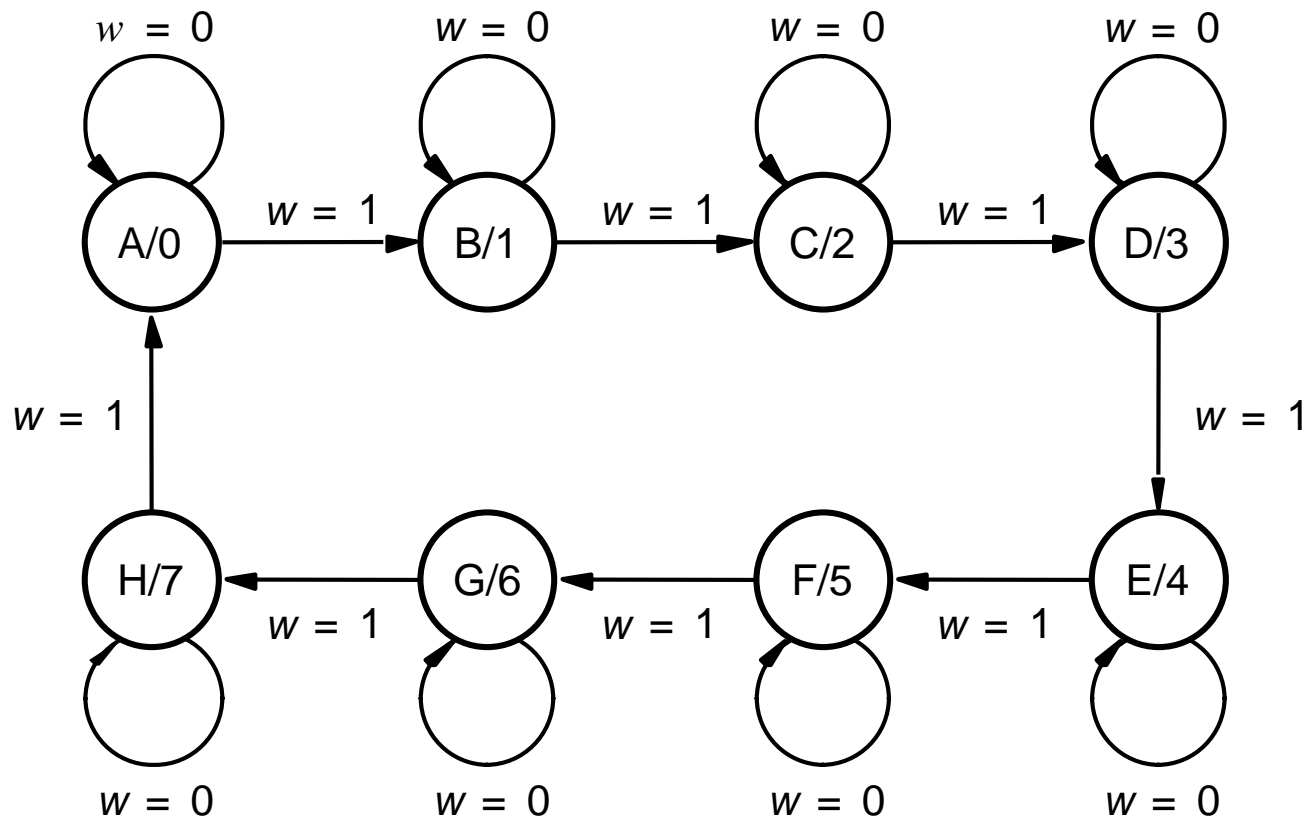

Modulo-8 Counter

Present state	Next state		Output
	$w = 0$	$w = 1$	
A	A	B	0
B	B	C	1
C	C	D	2
D	D	E	3
E	E	F	4
F	F	G	5
G	G	H	6
H	H	A	7

Modulo-8 Counter

	Present state $y_2y_1y_0$	Next state		Count $z_2z_1z_0$
		$w = 0$	$w = 1$	
		$Y_2Y_1Y_0$	$Y_2Y_1Y_0$	
A	000	000	001	000
B	001	001	010	001
C	010	010	011	010
D	011	011	100	011
E	100	100	101	100
F	101	101	110	101
G	110	110	111	110
H	111	111	000	111

Modulo-8 Counter

$y_1 y_0$					
$w y_2$		00	01	11	10
	00	0	1	1	0
	01	0	1	1	0
	11	1	0	0	1
	10	1	0	0	1

$$Y_0 = \bar{w}y_0 + w\bar{y}_0$$

$y_1 y_0$					
$w y_2$		00	01	11	10
	00	0	0	1	1
	01	0	0	1	1
	11	0	1	0	1
	10	0	1	0	1

$$Y_1 = \bar{w}y_1 + y_1\bar{y}_0 + w y_0\bar{y}_1$$

$y_1 y_0$					
$w y_2$		00	01	11	10
	00	0	0	0	0
	01	1	1	1	1
	11	1	1	0	1
	10	0	0	1	0

$$Y_2 = \bar{w}y_2 + \bar{y}_0y_2 + \bar{y}_1y_2 + w y_0y_1\bar{y}_2$$