



**DO NOT SHARE
SLIDES AND CLASS MATERIALS
ON ONLINE SITES**

Course Home

Advanced Logic Design

Computer Arithmetic: Distributed Arithmetic

Mingoo Seok
Columbia University

Readings:

Stanley A. White, “Applications of Distributed Arithmetic to Digital Signal Processing: A Tutorial Review,” IEEE ASSP Magazine, July, 1989

Xilinx App Note, ”The Role of Distributed Arithmetic In FPGA Based Signal Processing’

Distributed Arithmetic (DA)

- An efficient technique for calculation of **sum of products** or **vector dot product** or **inner product** or **multiply and accumulate** (MAC)
- MAC operation is very common in all Digital Signal Processing Algorithms
- Initially proposed by Peled and Liu in 1974

So Why Use DA?

- The advantages of DA are best exploited in designing data-path circuits
- Area savings from using DA can be up to 80% and seldom less than 50% in digital signal processing hardware designs
- An old technique that has been revived by the wide spread use of Field Programmable Gate Arrays (FPGAs) for Digital Signal Processing (DSP)
- DA efficiently implements the MAC using basic building blocks (Look Up Tables) in FPGAs

An Illustration of MAC Operation

- The following expression represents a multiply and accumulate operation

$$y = A_1 \times x_1 + A_2 \times x_2 + \square + A_K \times x_K$$

$$i.e. \quad y = \sum_{k=1}^K A_k x_k$$

- A numerical example

$$A = [32, 42, 45, 23] \quad x = [42, 20, -22, 67] \quad (K = 4)$$

$$y = 32 \times 42 + 45 \times 20 + 78 \times (-22) + 23 \times 67$$

$$y = 1344 + 900 - 1716 + 1541 = 2069$$

A Few Points about the MAC

- Consider this


$$y = \sum_{k=1}^K A_k x_k$$

Note a few points

- $A=[A_1, A_2, \dots, A_K]$ is a matrix of “**constant**” values
- $x=[x_1, x_2, \dots, x_K]$ is a matrix of input “**variables**”
- Each A_k is of M-bits
- Each x_k is of N-bits
- y should be large enough to accommodate the result

A Possible Hardware (not DA yet)

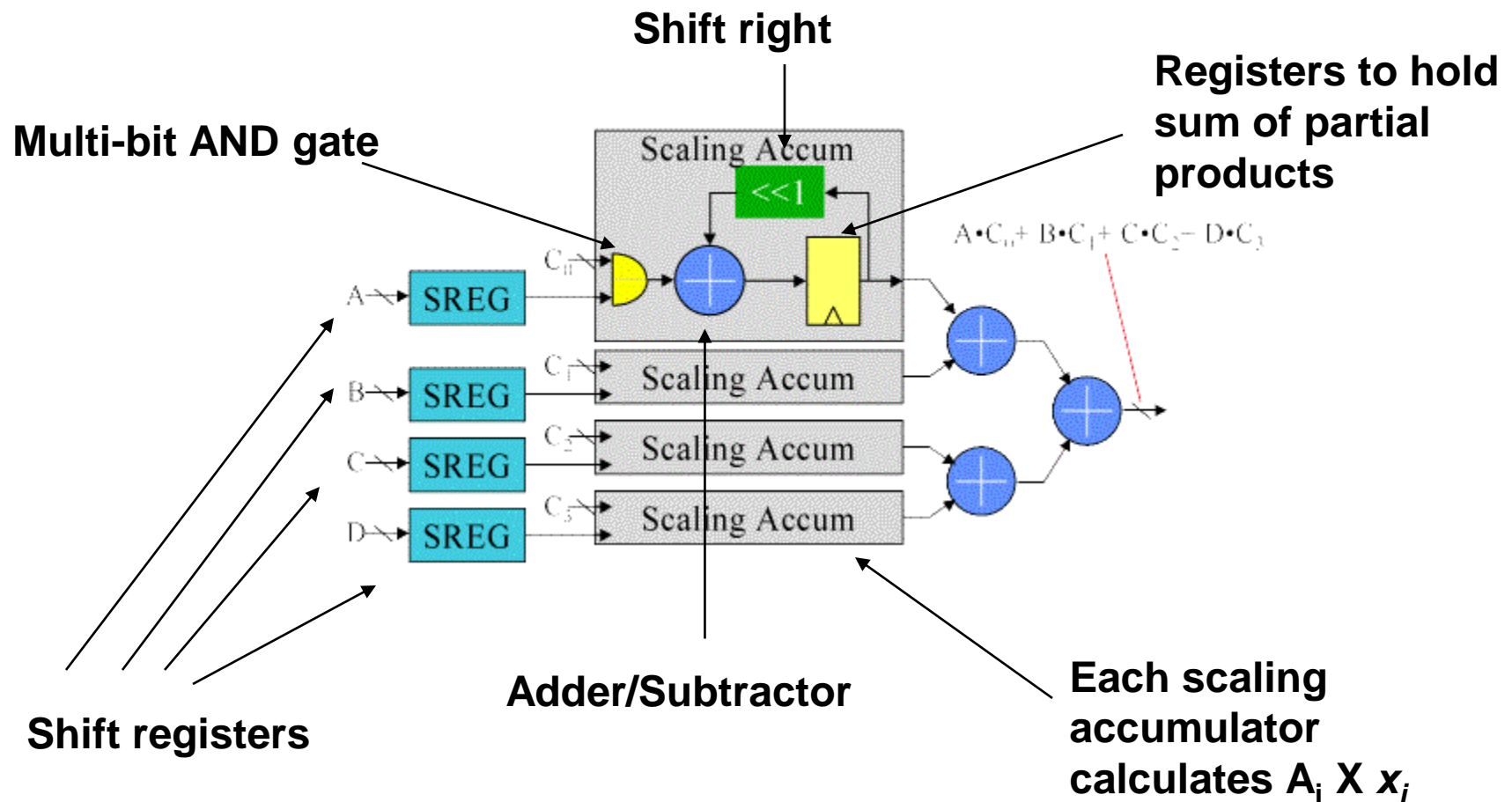■ Let, $A = [C_0, C_1, C_2, C_3]$ $x = [A, B, C, D]$ ($K = 4$)



How does DA work?

- The DA technique is **bit-serial**
- DA is basically a **bit-level rearrangement** of the multiply and accumulate operation
 - Try to replace a multiplier with a LUT
 - The size of address will be the size of the constant vector, (e.g., 4 in the previous example)
- DA hides the explicit multiplications by **LUT**
 - An efficient technique to implement on Field Programmable Gate Arrays (FPGAs)
 - Because FPGAs are a collection of LUTs

Moving Closer to Distributed Arithmetic

- Consider once again $y = \sum_{k=1}^K A_k x_k \quad \dots(1)$
- Let x_k be a N-bits scaled two's complement number i.e.

$$|x_k| < 1$$

$$x_k: \{b_{k0}, b_{k1}, b_{k2}, \dots, b_{k(N-1)}\}$$

where b_{k0} is the *sign bit*

- We can express x_k as $x_k = -b_{k0} + \sum_{n=1}^{N-1} b_{kn} 2^{-n} \quad \dots(2)$
- Substituting (2) in (1),

$$y = \sum_{k=1}^K A_k \left[-b_{k0} + \sum_{n=1}^{N-1} b_{kn} 2^{-n} \right]$$

$$y = -\sum_{k=1}^K (b_{k0} \bullet A_k) + \sum_{k=1}^K \sum_{n=1}^{N-1} (A_k \bullet b_{kn}) 2^{-n} \quad \dots(3)$$

Moving More Closer to DA

$$y = -\sum_{k=1}^K (b_{k0} \bullet A_k) + \sum_{k=1}^K \underbrace{\left[\sum_{n=1}^{N-1} (b_{kn} \bullet A_k) 2^{-n} \right]} \dots (3)$$

Expanding this part

$$y = -\underbrace{\sum_{k=1}^K (b_{k0} \bullet A_k)} + \underbrace{\sum_{k=1}^K \left[(A_k \bullet b_{k1}) 2^{-1} + (A_k \bullet b_{k2}) 2^{-2} + \square + (A_k \bullet b_{k(N-1)}) 2^{-(N-1)} \right]}$$

$$y = -\left[b_{10} \bullet A_1 + b_{20} \bullet A_2 + \square + b_{K0} \bullet A_K \right]$$

$$+ \left[(b_{11} \bullet A_1) 2^{-1} + (b_{12} \bullet A_1) 2^{-2} + \square + (b_{1(N-1)} \bullet A_1) 2^{-(N-1)} \right]$$

$$+ \left[(b_{21} \bullet A_2) 2^{-1} + (b_{22} \bullet A_2) 2^{-2} + \square + (b_{2(N-1)} \bullet A_2) 2^{-(N-1)} \right]$$

$$\square$$

$$+ \left[(b_{K1} \bullet A_K) 2^{-1} + (b_{K2} \bullet A_K) 2^{-2} + \square + (b_{K(N-1)} \bullet A_K) 2^{-(N-1)} \right]$$

Moving Still More Closer to DA

$$\begin{aligned}
 y = & -[b_{10} \bullet A_1 + b_{20} \bullet A_2 + \square + b_{K0} \bullet A_K] \\
 & + [(b_{11} \bullet A_1)2^{-1} + (b_{12} \bullet A_1)2^{-2} + \square + (b_{1(N-1)} \bullet A_1)2^{-(N-1)}] \\
 & + [(b_{21} \bullet A_2)2^{-1} + (b_{22} \bullet A_2)2^{-2} + \square + (b_{2(N-1)} \bullet A_2)2^{-(N-1)}] \\
 & + [(b_{K1} \bullet A_K)2^{-1} + (b_{K2} \bullet A_K)2^{-2} + \square + (b_{K(N-1)} \bullet A_K)2^{-(N-1)}]
 \end{aligned}$$

$$\begin{aligned}
 y = & -[b_{10} \bullet A_1 + b_{20} \bullet A_2 + \square + b_{K0} \bullet A_K] \\
 & + [(b_{11} \bullet A_1) + (b_{21} \bullet A_2) + \square + (b_{K1} \bullet A_K)]2^{-1} \\
 & + [(b_{12} \bullet A_1) + (b_{22} \bullet A_2) + \square + (b_{K2} \bullet A_K)]2^{-2} \\
 & + [(b_{1(N-1)} \bullet A_1) + (b_{2(N-1)} \bullet A_2) + \square + (b_{K(N-1)} \bullet A_K)]2^{-(N-1)}
 \end{aligned}$$

Almost there!

$$y = -[b_{10} \bullet A_1 + b_{20} \bullet A_2 + \square + b_{K0} \bullet A_K] \\ + [(b_{11} \bullet A_1) + (b_{21} \bullet A_2) + \square + (b_{K1} \bullet A_K)]2^{-1} \\ + [(b_{12} \bullet A_1) + (b_{22} \bullet A_2) + \square + (b_{K2} \bullet A_K)]2^{-2} \\ \square \\ + [(b_{1(N-1)} \bullet A_1) + (b_{2(N-1)} \bullet A_2) + \square + (b_{K(N-1)} \bullet A_K)]2^{-(N-1)}$$


$$y = -\sum_{k=1}^K (b_{k0}) \bullet A_k + \sum_{n=1}^{N-1} [b_{1n} \bullet A_k + b_{2n} \bullet A_2 + \square + b_{Kn} \bullet A_K]2^{-n}$$

$$y = -\sum_{k=1}^K A_k \bullet (b_{k0}) + \sum_{n=1}^{N-1} \left[\sum_{k=1}^K A_k \bullet b_{kn} \right] 2^{-n} \quad \dots(4)$$


The Final Reformulation

Lets See the change of hardware

 
$$y = -\sum_{k=1}^K (b_{k0} \cdot A_k) + \sum_{k=1}^K \sum_{n=1}^{N-1} (b_{kn} \cdot A_k) 2^{-n}$$




Our Original Equation

 


 
$$y = -\sum_{k=1}^K A_k \cdot (b_{k0}) + \sum_{n=1}^{N-1} \left[\sum_{k=1}^K A_k \cdot b_{kn} \right] 2^{-n}$$



Bit Level Rearrangement

 

So where does the ROM come in?

 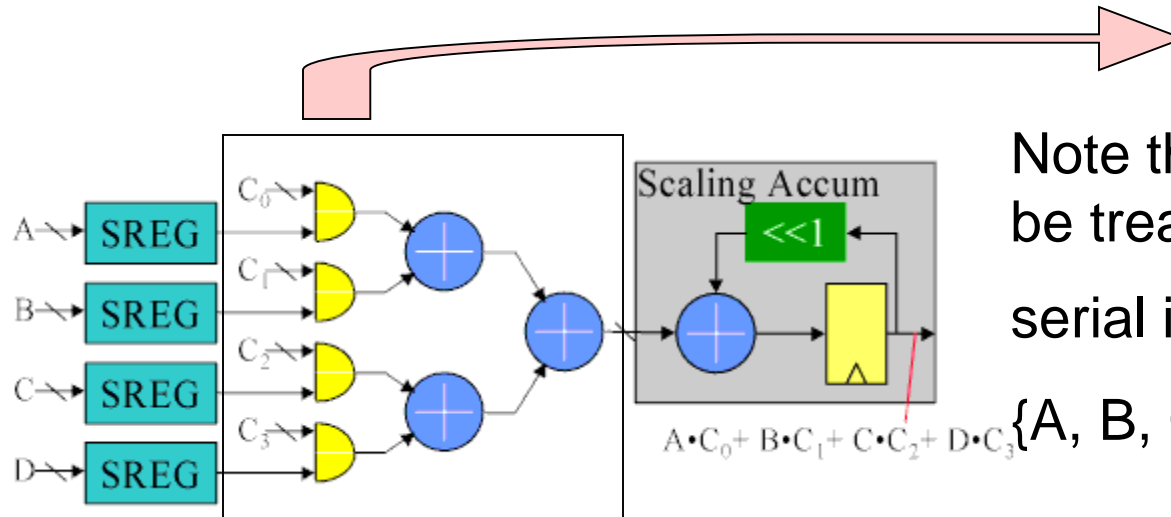

The ROM Construction

$$y = -\sum_{k=1}^K A_k \bullet (b_{k0}) + \sum_{n=1}^{N-1} \left[\sum_{k=1}^K A_k \bullet b_{kn} \right] 2^{-n} \quad \dots (4)$$

- $\left[\sum_{k=1}^K A_k b_{kn} \right]$ has only(?) 2^K possible values i.e.

$$\left[\sum_{k=1}^K A_k b_{kn} \right] = f_n(b_{1n} b_{2n} \dots b_{Kn}) \quad \dots (5)$$

- (5) can be **pre-calculated** for all possible values of $b_{1n} b_{2n} \dots b_{Kn}$
- We can store these in a look-up table of **2^K words** addressed by **K -bits** i.e. $b_{1n} b_{2n} \dots b_{Kn}$

Lets See An Example

- Let number of taps $K=4$
- The fixed coefficients are $A_1=0.72$, $A_2=-0.3$, $A_3=0.95$, $A_4=0.11$

$$y = \sum_{n=1}^{N-1} \left[\underbrace{\sum_{k=1}^K A_k b_{kn}}_{\text{}} \right] 2^{-n} + \underbrace{\sum_{k=1}^K A_k (-b_{k0})}_{\text{}} \dots (4)$$

- We need $2^K = 2^4 = 16$ -words ROM

ROM: Address and Contents



$$\left[\sum_{k=1}^4 A_k b_{kn} \right] = A_1 b_{1n} + A_2 b_{2n} + A_3 b_{3n} + A_4 b_{4n}$$

b_{1n}	b_{2n}	b_{3n}	b_{4n}	Contents
0	0	0	0	0
0	0	0	1	$A_4=0.11$
0	0	1	0	$A_3=0.95$
0	0	1	1	$A_3 + A_4=1.06$
0	1	0	0	$A_2=-0.30$
0	1	0	1	$A_2 + A_4 = -0.19$
0	1	1	0	$A_2 + A_3=0.65$
0	1	1	1	$A_2 + A_3 + A_4=0.75$
1	0	0	0	$A_1=0.72$
1	0	0	1	$A_1 + A_4=0.83$
1	0	1	0	$A_1 + A_3=1.67$
1	0	1	1	$A_1 + A_3 + A_4=1.78$
1	1	0	0	$A_1 + A_2=0.42$
1	1	0	1	$A_1 + A_2 + A_4=0.53$
1	1	1	0	$A_1 + A_2 + A_3=1.37$
1	1	1	1	$A_1 + A_2 + A_3 + A_4=1.48$

Key Issue: ROM Size

- The size of ROM is very important for high speed implementation as well as area efficiency
- ROM size grows exponentially with each added input address line
- The number of address lines are equal to the number of elements in the vector of constants i.e. K
- Elements up to 16 and more are common => $2^{16}=64\text{K}$ -words of ROM (!)
- We have to reduce the size of ROM

Decomposing the ROM

 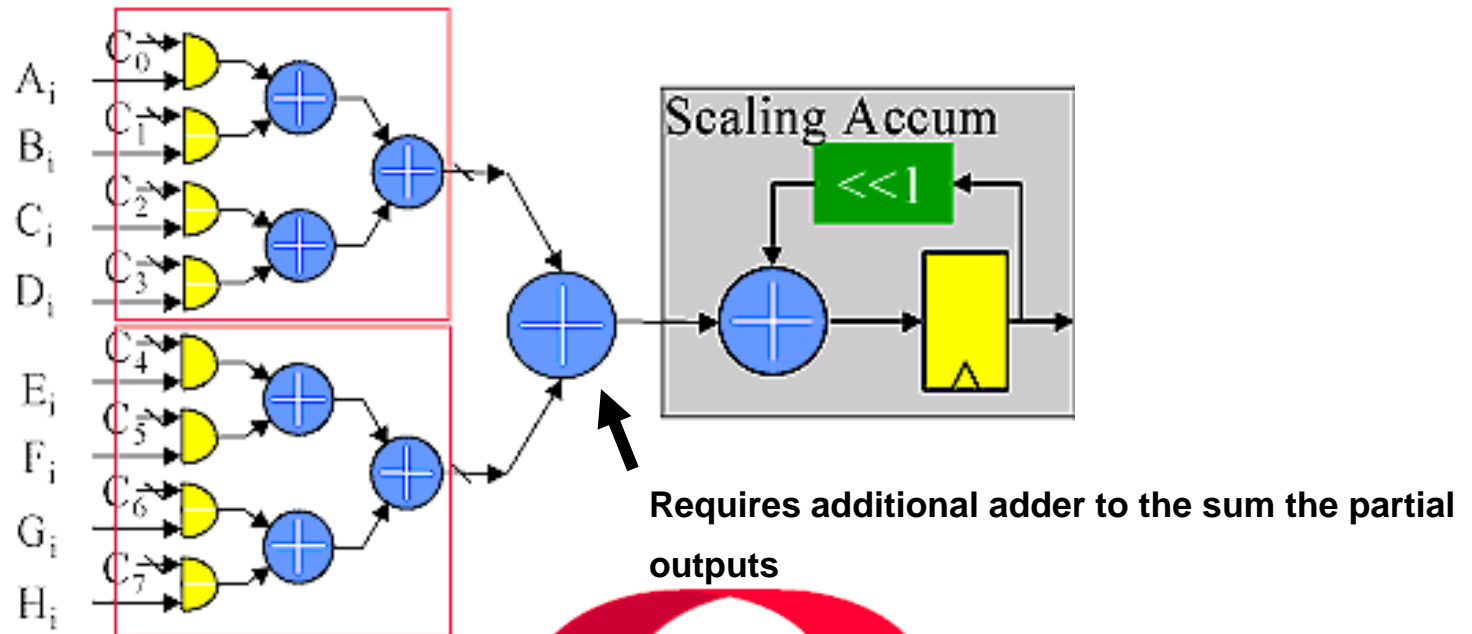

Addr	Data
0000	0
0001	C_0
0010	C_1
0011	$C_0 + C_1$
\vdots	\vdots
1110	$C_1 + C_2 + C_3$
1111	$C_0 + C_1 + C_2 + C_3$

Speed Concerns

- We considered One Bit At A Time (1 BAAT)
- No. of Clock Cycles Required = N
- If $K=N$, then essentially we are taking 1 cycle per dot product. Not bad!
- Opportunity for parallelism exists but at a cost of more hardware
- We could have 2 BAAT or up to N BAAT in the extreme case
- N BAAT. One complete result/cycle

Illustration of 2 BAAT

 


Illustration of N BAAT (N=4)

