



**DO NOT SHARE
SLIDES AND CLASS MATERIALS
ON ONLINE SITES**
Course Hero

CSEE W4823 Advanced Logic Design
Homework Assignment #1

1. A four-variable logic function that is equal to 1 if any three or all four of its variables are equal to 1 is called a *majority* function. Design a minimum-cost SOP circuit that implements this majority function

2. Convert the following decimal numbers into binary

- (a) 17
- (b) 33
- (c) 67
- (d) 130
- (e) 2560
- (f) 51200

3. Convert the decimal fraction 0.8254 into a binary representation.

4. For the flip-flops in the counter in the figure below assume that $t_{su} = 3$ ns, $t_h = 1$ ns, and the propagation delay through a flip-flop is 1 ns. Assume that each AND gate, XOR gate, and 2-to-1 multiplexer has a propagation delay equal to 1 ns. What is the maximum clock frequency for which the circuit will operate correctly?

