



**DO NOT SHARE
SLIDES AND CLASS MATERIALS
ON ONLINE SITES**

Course Home


Advanced Logic Design

Algorithmic State Machines (ASM) Method


Mingoo Seok
Columbia University

BV: Secs. 6.10-6.13, 7.3-7.4


Algorithmic State Machine

 


(a) State box

 


(b) Example of state box

 

(c) Decision box


 


(d) Conditional output box

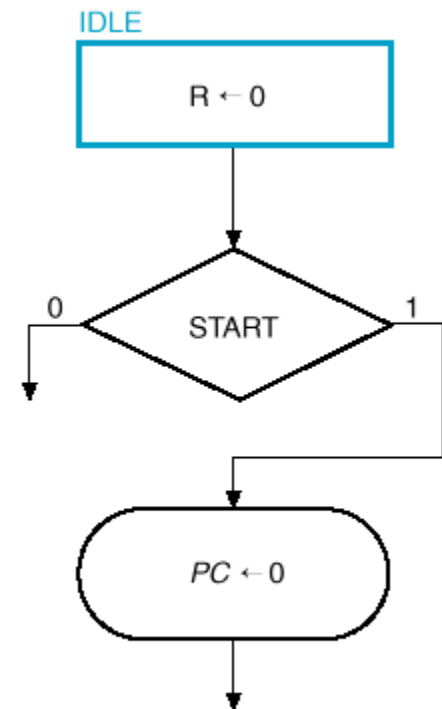

(e) Example of decision and condition output box


ASM Chart Example

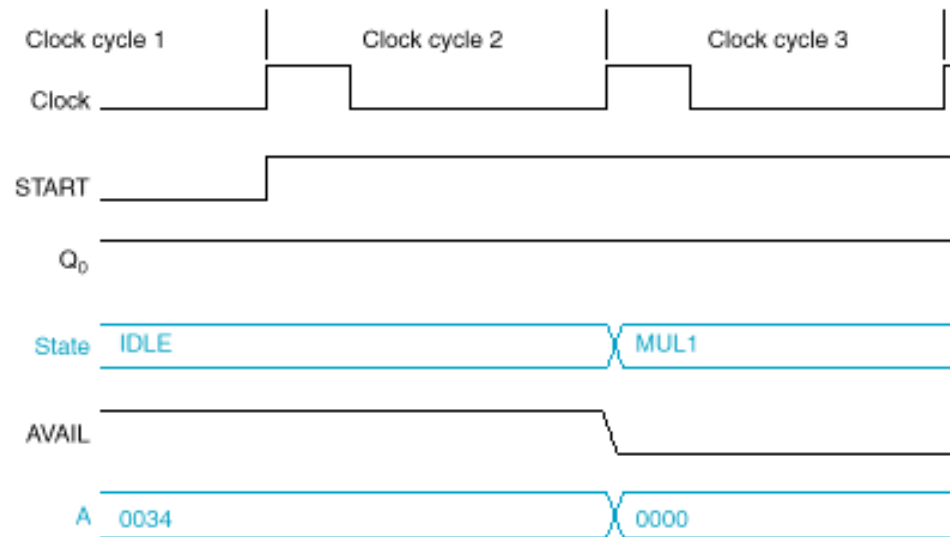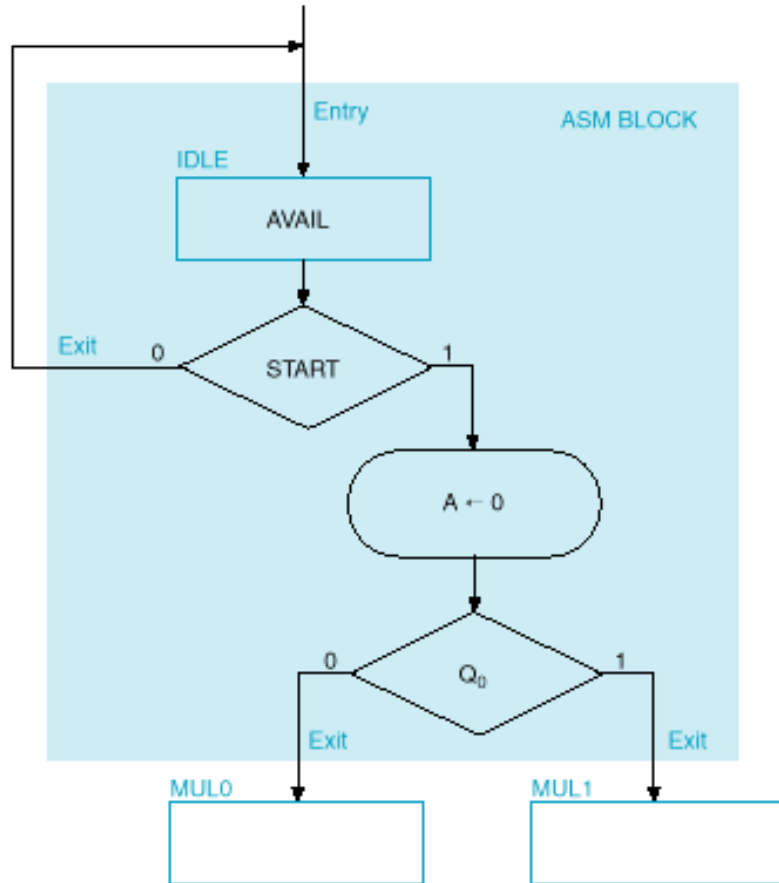



Bit Counting Circuit

```

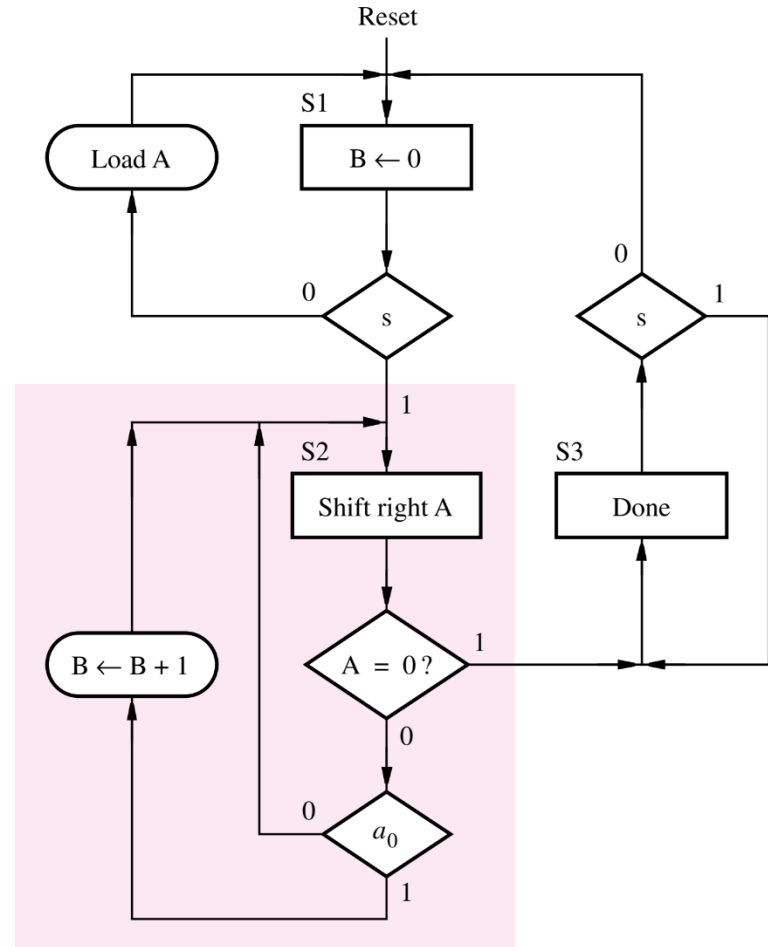
 $B = 0;$ 
while  $A \neq 0$  do
  if  $a_0 = 1$  then
     $B = B + 1;$ 
  end if;
  Right-shift A;
end while;
    
```





Timing Implied in ASM

 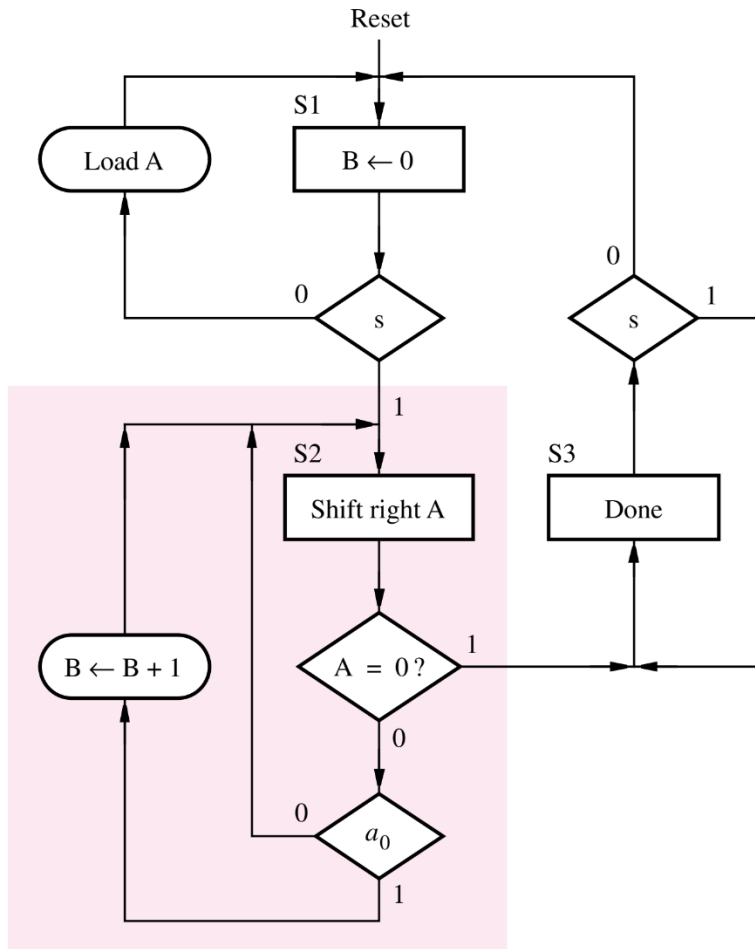

Datapath

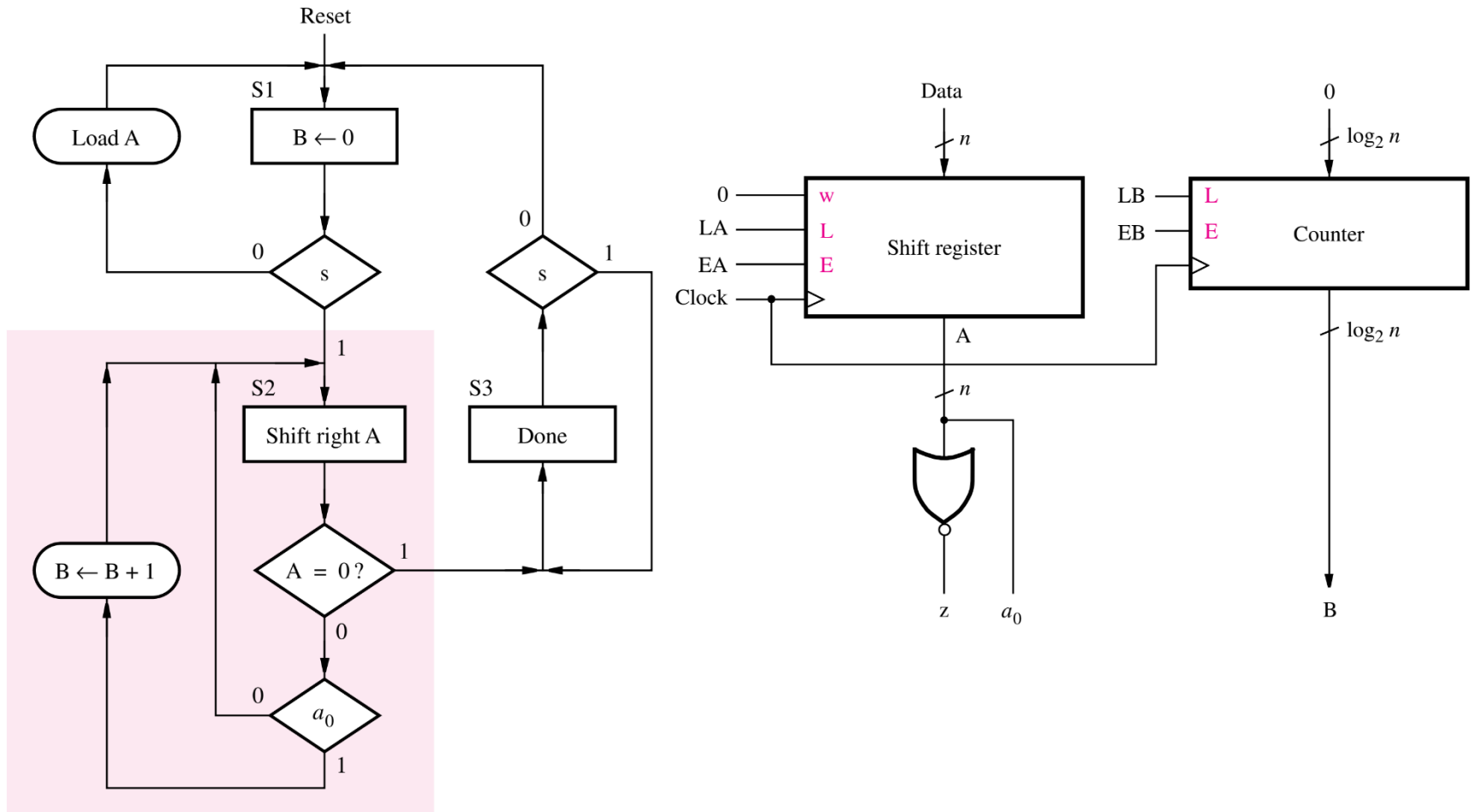

Control

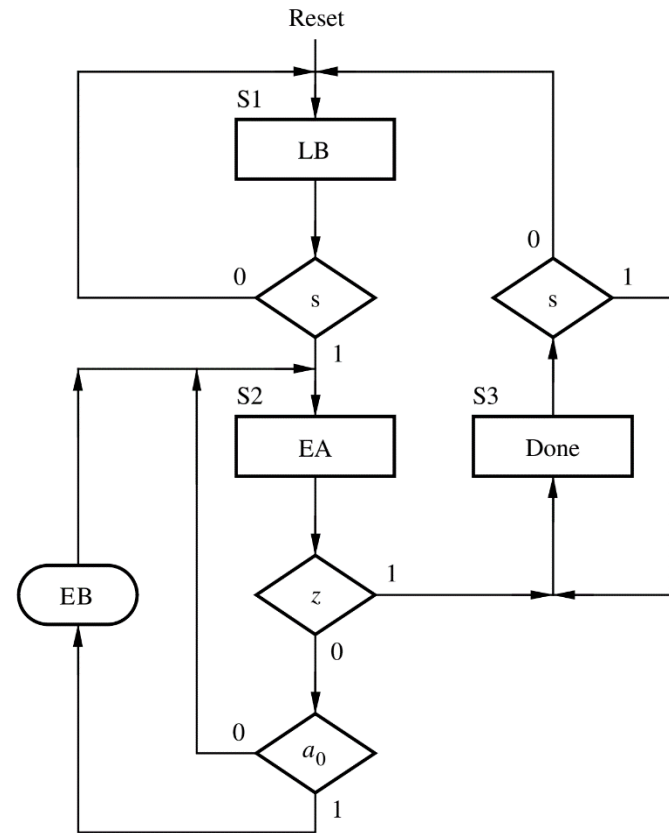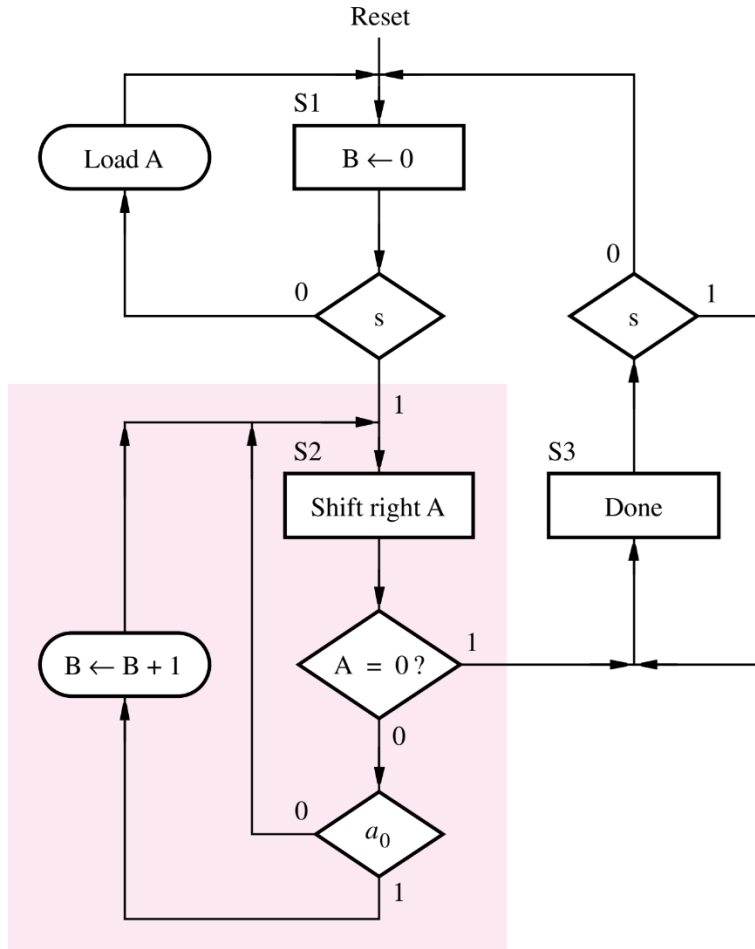

Verilog HDL Code

```
module bitcount (Clock, Resetn, LA, s, Data, B, Done);
  input Clock, Resetn, LA, s;
  input [7:0] Data;
  output reg [3:0] B;
  output reg Done;
  wire [7:0] A;
  wire z;
  reg [1:0] Y, y;
  reg EA, EB, LB;

  // control circuit

  parameter S1 = 2'b00, S2 = 2'b01, S3 = 2'b10;

  always @(s, y, z)
  begin: State_table
    case (y)
      S1: if (!s) Y = S1;
          else Y = S2;
      S2: if (z == 0) Y = S2;
          else Y = S3;
      S3: if (s) Y = S3;
          else Y = S1;
      default: Y = 2'bxx;
    endcase
  end

  always @(posedge Clock, negedge Resetn)
  begin: State_flipflops
    if (Resetn == 0)
      y <= S1;
    else
      y <= Y;
  end
```

```
  always @(y, A[0])
  begin: FSM_outputs
    // defaults
    EA = 0; LB = 0; EB = 0; Done = 0;
    case (y)
      S1: LB = 1;
      S2: begin
          EA = 1;
          if (A[0]) EB = 1;
          else EB = 0;
        end
      S3: Done = 1;
    endcase
  end

  // datapath circuit

  // counter B
  always @(negedge Resetn, posedge Clock)
  if (!Resetn)
    B <= 0;
  else if (LB)
    B <= 0;
  else if (EB)
    B <= B + 1;

  shiftreg ShiftA (Data, LA, EA, 1'b0, Clock, A);
  assign z = ~ | A;

endmodule
```

Shift-and-Add Multiplier

Decimal	Binary	
13	1 1 0 1	Multiplicand
$\times 11$	$\times 1 0 1 1$	Multiplier
<hr/>	1 1 0 1	
13	1 1 0 1	
13	0 0 0 0	
<hr/>	1 1 0 1	
143	1 0 0 0 1 1 1 1	Product

(a) Manual method

```

P = 0 ;
for i = 0 to n - 1 do
    if  $b_i = 1$  then
         $P = P + A$  ;
    end if;
    Left-shift A ;
end for;
    
```


(b) Pseudo-code

- For large words, the array multiplier can be too hardware intensive
- Implement a *multi-cycle* multiplier with a shifter and an adder



Pseudo Code to ASM Chart

```


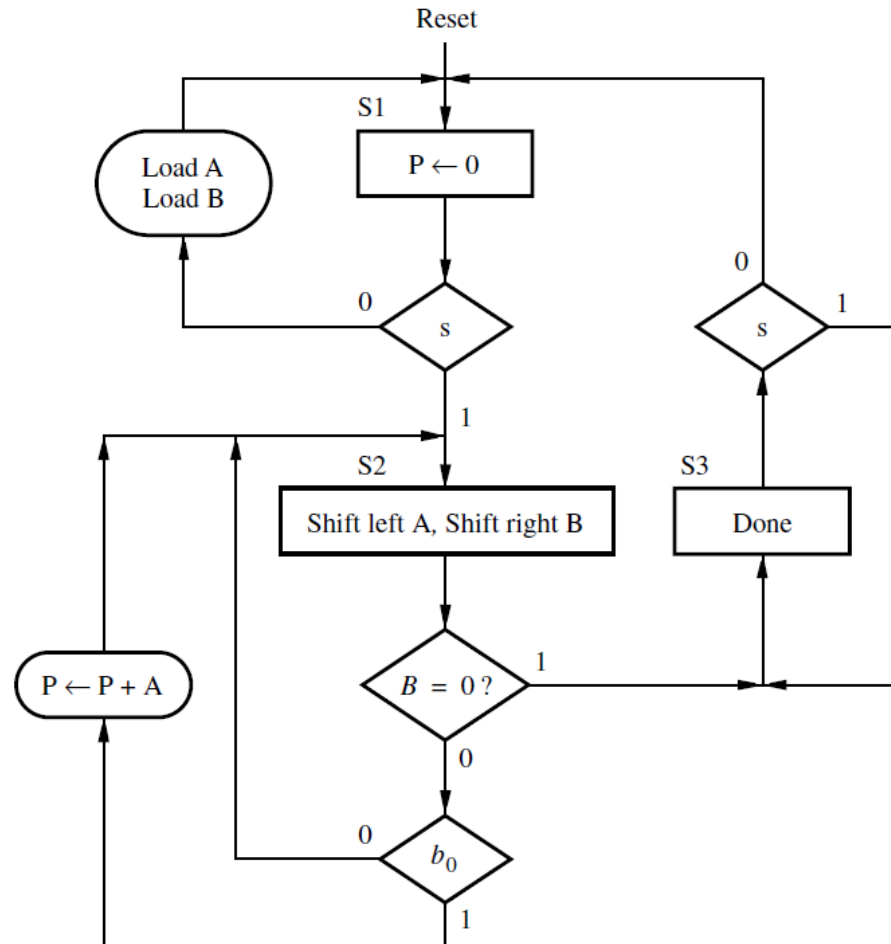
P ← 0 ;
for i = 0 to n - 1 do
    if bi = 1 then
        P ← P + A ;
    end if;
    Left-shift A ;
end for;
    
```



ASM to Datapath

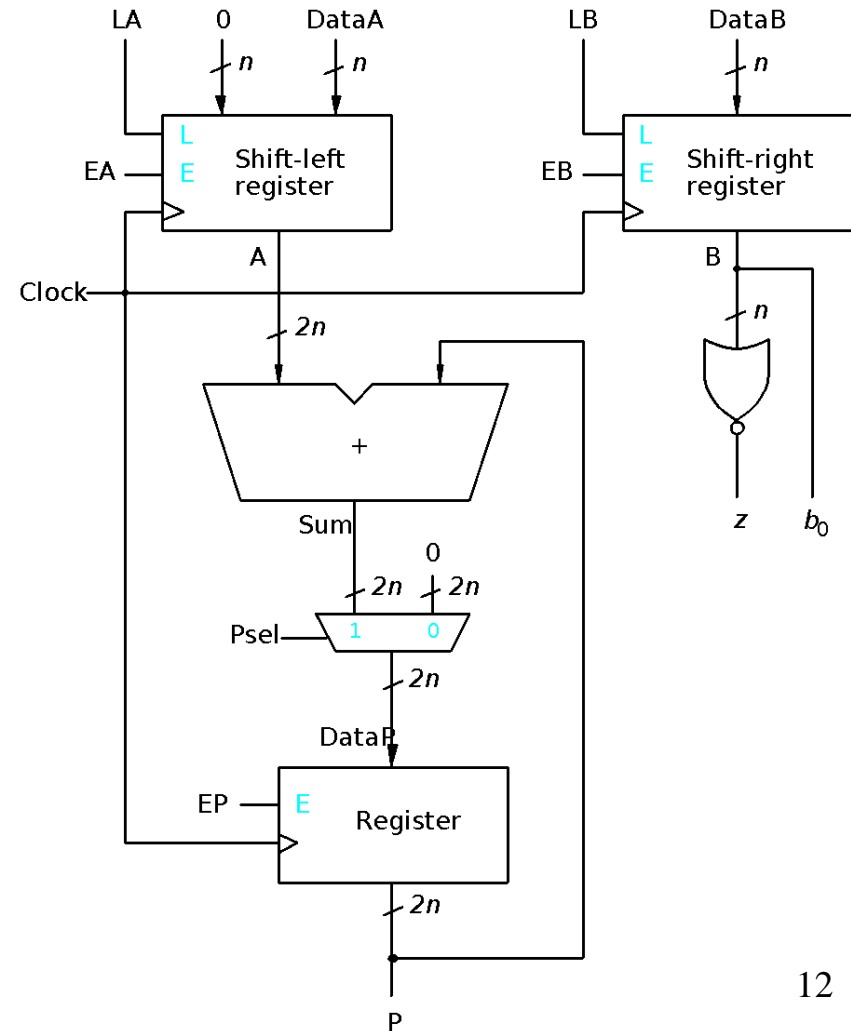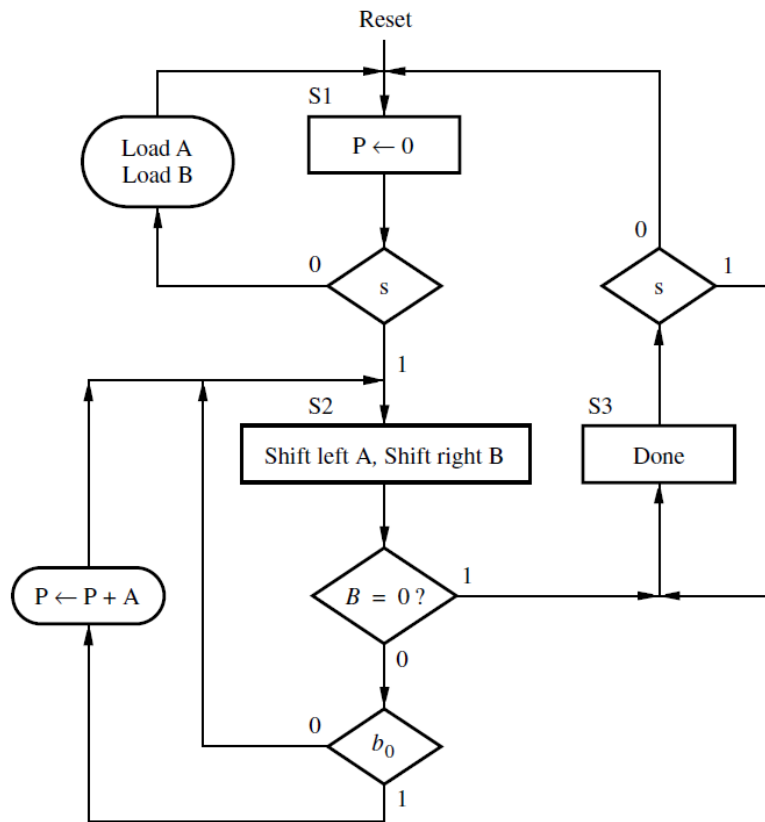

ASM to Control ASM

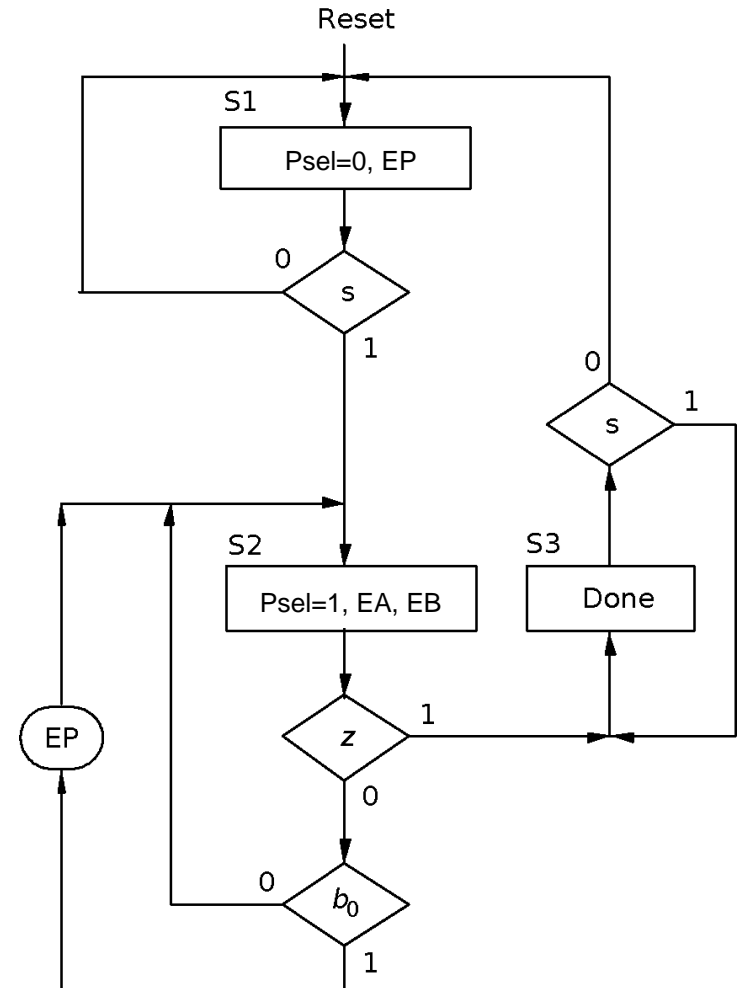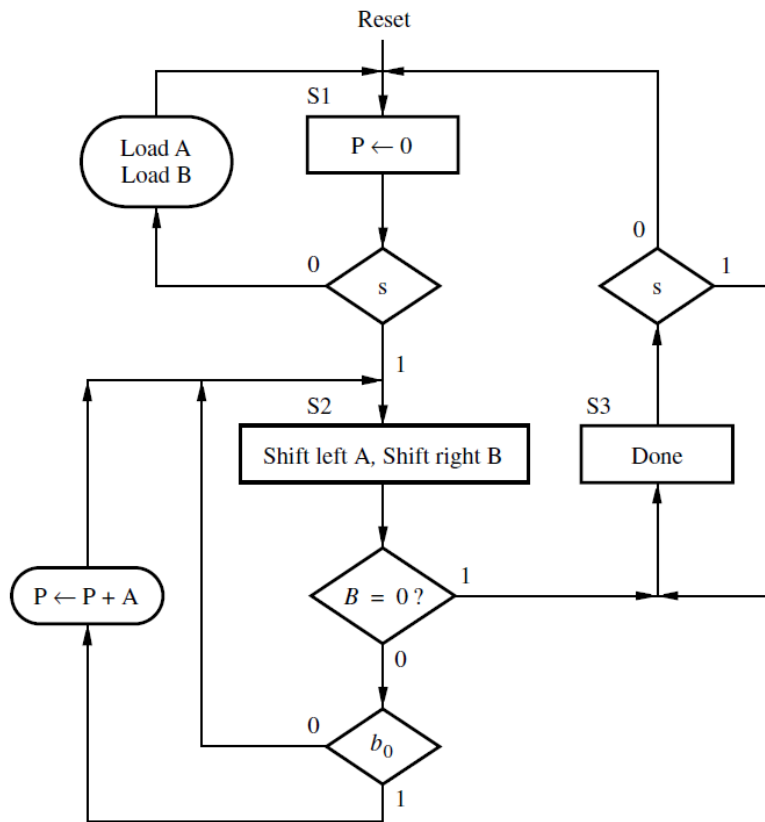

Control ASM to Verilog

```
module multiply (Clock, Resetn, LA, LB, s, DataA, DataB, P, Done);
```

```
    parameter n = 8;
    input Clock, Resetn, LA, LB, s;
    input [n-1:0] DataA, DataB;
    output [n+n-1:0] P;
    output reg Done;
    wire z;
    reg [n+n-1:0] A, DataP;
    wire [n+n-1:0] Sum;
    reg [1:0] y, Y;
    reg [n-1:0] B;
    reg EA, EB, EP, Psel;
    integer k;
```

```
// control circuit
```

```
    parameter S1 = 2'b00, S2 = 2'b01, S3 = 2'b10;
```

```
    always @(s, y, z)
    begin: State_table
```

```
        case (y)
        S1:      if (s == 0) Y = S1;
                  else Y = S2;
        S2:      if (z == 0) Y = S2;
                  else Y = S3;
        S3:      if (s == 1) Y = S3;
                  else Y = S1;
                  default: Y = 2'bxx;
        endcase
```

```
    end
```

```
    always @(posedge Clock, negedge Resetn)
```

```
    begin: State_flipflops
        if (Resetn == 0)
            y <= S1;
        else
            y <= Y;
```

```
    end
```

```
//datapath circuit
```

```
    always @(s, y, B[0])
```

```
    begin: FSM_outputs
```

```
        // defaults
```

```
        EA = 0; EB = 0; EP = 0; Done = 0; Psel = 0;
```

```
        case (y)
```

```
        S1: EP = 1;
```

```
        S2: begin
```

```
            EA = 1; EB = 1; Psel = 1;
```

```
            if (B[0]) EP = 1;
```

```
            else EP = 0;
```

```
        end
```

```
        S3: Done = 1;
```

```
    endcase
```

```
    end
```

```
    shiftrne ShiftB (DataB, LB, EB, 0, Clock, B);
```

```
        defparam ShiftB.n = 8;
```

```
    shiftlne ShiftA ({ {n{1'b0}}, DataA}, LA, EA, 1'b0, Clock, A);
```

```
        defparam ShiftA.n = 16;
```

```
    assign z = (B == 0);
```

```
    assign Sum = A + P;
```

```
// define the 2n 2-to-1 multiplexers
```

```
    always @(Psel, Sum)
```

```
        for (k = 0; k < n+n; k = k+1)
```

```
            DataP[k] = Psel ? Sum[k] : 1'b0;
```

```
    regne RegP (DataP, Clock, Resetn, EP, P);
```

```
        defparam RegP.n = 16;
```

```
endmodule
```

$$\begin{array}{r} 15 \\ 9 \overline{) 140} \\ \underline{9} \\ 50 \\ \underline{45} \\ 5 \end{array}$$

$$\begin{array}{r}
 \begin{array}{c} \text{B} \longrightarrow 1001 \end{array} \overline{) \begin{array}{c} 00001111 \\ 10001100 \\ \hline 1001 \\ 10001 \\ \hline 1001 \\ 10000 \\ \hline 1001 \\ 1110 \\ \hline 1001 \\ 101 \end{array} }
 \end{array}
 \begin{array}{l}
 \longleftarrow \text{Q} \\
 \longleftarrow \text{A} \\
 \\
 \\
 \\
 \\
 \\
 \\
 \longleftarrow \text{R}
 \end{array}$$

```

 $R = 0;$ 
for  $i = 0$  to  $n - 1$  do
    Left-shift  $R \parallel A;$ 
    if  $R \geq B$  then
         $q_i = 1;$ 
         $R = R - B;$ 
    else
         $q_i = 0;$ 
    end if;
end for;


```

Algorithm to ASM



```

 $R = 0;$ 
for  $i = 0$  to  $n - 1$  do
    Left-shift  $R \parallel A$ ;
    if  $R \geq B$  then
         $q_i = 1;$ 
         $R = R - B;$ 
    else
         $q_i = 0;$ 
    end if;
end for;

```

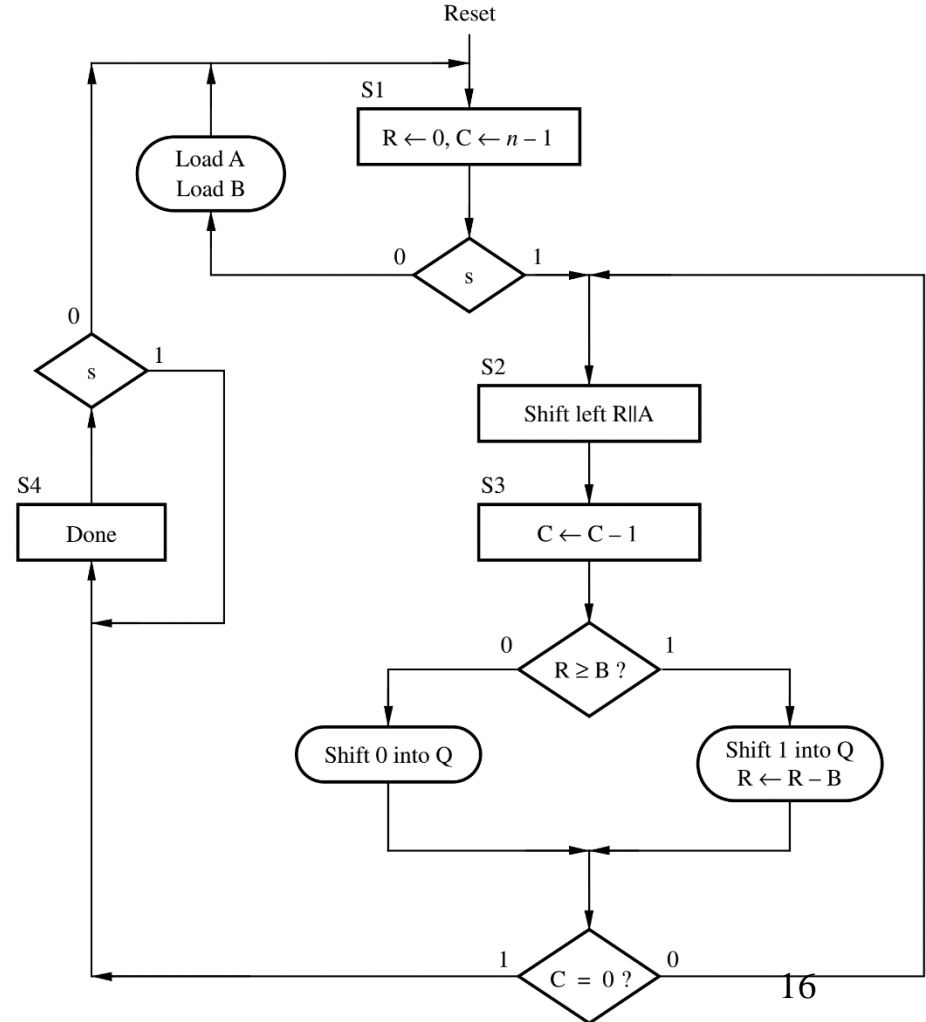

ASM to Datapath Circuit

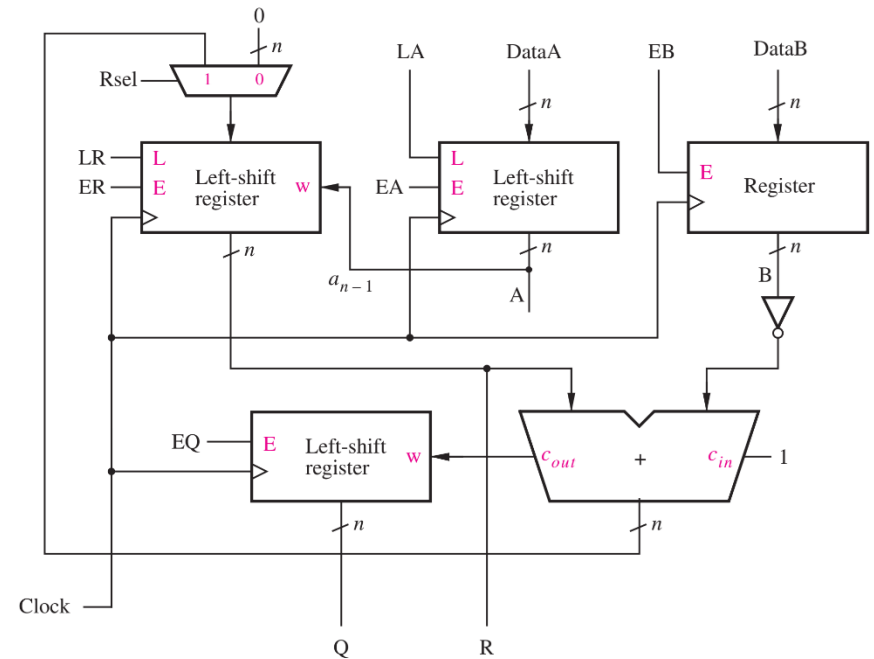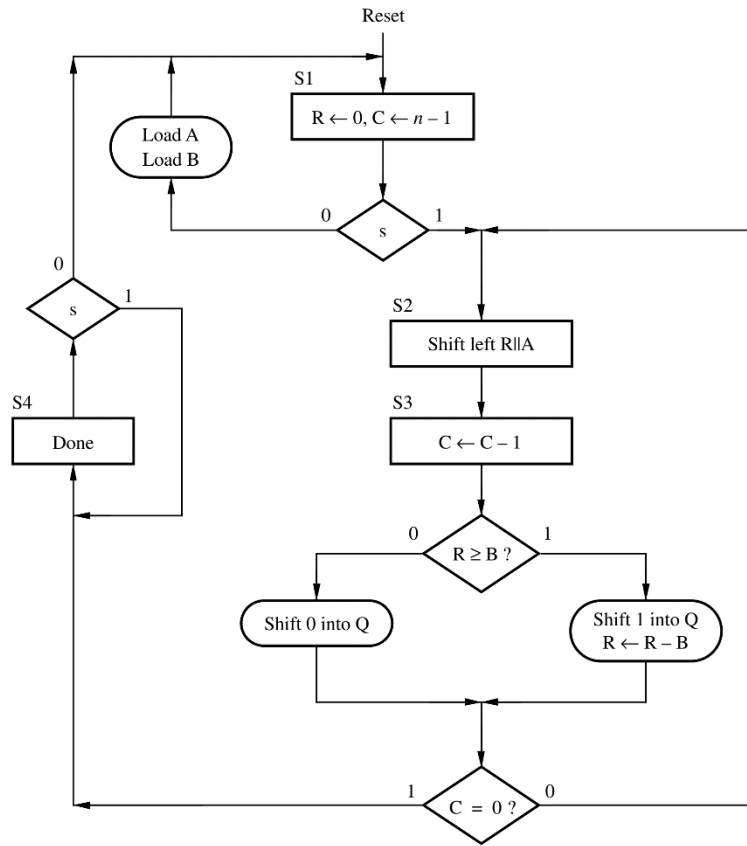

ASM to Control ASM

